

Homework Problems

Transistor Bias Design and Analysis and Amplifier Analysis

rev 2

Note: Problems 6 to 10 are answers to problems 1 to 5 with rounding to nearest standard values. For problems 1 through 5, calculate R_E , R_{B1} , and R_{B2} . $V_{BE} = 0.65$ @ 25 deg. C and has a temperature coefficient of -0.0022 Volts/degree C. Use $K_T = K_B = 1.2$. All circuits use a NPN transistor operating on a single supply of V_{CC} ($V_{EE} = 0$).

Bias design problems:

1. $T_{min} = 10$, $T_{max} = 40$, $B_{min} = 30$, $B_{max} = 100$, $V_{CC} = 3$, $I_C = 5$ mA.
2. $T_{min} = 0$, $T_{max} = 50$, $B_{min} = 40$, $B_{max} = 150$, $V_{CC} = 5$, $I_C = 10$ mA.
3. $T_{min} = 10$, $T_{max} = 40$, $B_{min} = 50$, $B_{max} = 200$, $V_{CC} = 9$, $I_C = 3$ mA,
4. $T_{min} = 0$, $T_{max} = 70$, $B_{min} = 80$, $B_{max} = 250$, $V_{CC} = 12$, $I_C = 1.5$ mA.
5. $T_{min} = -20$, $T_{max} = 60$, $B_{min} = 100$, $B_{max} = 300$, $V_{CC} = 20$, $I_C = 1$ mA.

Bias analysis problems: Use the nominal V_{BE} and Beta calculated from above.

6. $V_{CC} = 3$, $R_C = 200$, $R_E = 62$, $R_{B1} = 1.6K$, $R_{B2} = 820$
7. $V_{CC} = 5$, $R_C = 0$, $R_E = 51$, $R_{B1} = 2.2K$, $R_{B2} = 750$
8. $V_{CC} = 9$, $R_C = 1K$, $R_E = 110$, $R_{B1} = 13K$, $R_{B2} = 1.6K$
9. $V_{CC} = 12$, $R_C = 3.3K$, $R_E = 470$, $R_{B1} = 91K$, $R_{B2} = 13K$
10. $V_{CC} = 20$, $R_C = 8.2K$, $R_E = 820$, $R_{B1} = 300K$, $R_{B2} = 27K$

Amplifier analysis problems: Find R_{in} , R_o , A_v unloaded, net gain and power gain.

11. Use circuit from problem 6. Common-emitter connection with $R_{source} = 250$ Ohms and $R_{load} = 300$ Ohms.
12. Use circuit from problem 7. Common-collector connection with $R_{source} = 500$ Ohms and $R_{load} = 100$ Ohms.
13. Use circuit from problem 8. Common-base connection with $R_{source} = 10$ Ohms and $R_{load} = 1200$ Ohms.
14. Use circuit from problem 9. Common-emitter connection with $R_{source} = 2000$ Ohms and $R_{load} = 3000$ Ohms
15. Use circuit from problem 10. Common-base connection with $R_{source} = 40$ Ohms and $R_{load} = 10$ K.