

BJT Practice Problems

Oct. 8, 2012

All transistors have V_{BE} at 25 C = 0.65 volts and a -0.002 volt/C temperature coefficient. Use the transistor_designer.xlsx spreadsheet on the website to check your work. It provides all of the answers for both design and analysis. It is possible that some of the designs won't work – i.e. negative results – I have not had time to check all permutations – do not worry if that happens – it might happen once or not at all. These problems give plenty of practice doing bias design, AC design, bias analysis, and AC analysis.

1. Design a common-emitter amplifier to drive a load resistance of 2,000 ohms with an A_{vl} of -50 using optimum large signal design (V_{CQ} optimum). $T_{min} = 0$ C, $T_{max} = 60$ C, $B_{min} = 50$, $B_{max} = 200$, $K_T = 1.2$, $K_B = 1.2$, $V_{CBmin} = 2$ volts. Do three designs: (1) $V_{CC} = 6$ volts, $R_C = 1,000$ ohms; (2) $V_{CC} = 12$ volts, $R_C = 2,000$ ohms; (3) $V_{CC} = 24$ volts, $R_C = 3,900$ ohms. Do analysis on each of your designs to verify that the required V_{CQ} is met and that A_{vl} is met.
2. Design a common-collector amplifier to drive a load resistance of 500 ohms using optimum large signal design (V_{EQ} optimum). $B_{min} = 80$, $B_{max} = 250$, $K_B = 1.2$, do not worry about temperature, $V_{CEsat} = 0.2$ volts. Do three designs: (1) $V_{CC} = 6$ volts, $R_E = 270$ ohms; (2) $V_{CC} = 12$ volts, $R_E = 510$ ohms; (3) $V_{CC} = 24$ volts, $R_E = 1,000$ ohms. Do analysis on each of your designs to verify that the required V_{EQ} is met. Also calculate A_{vl} for each case.
3. Design a common-emitter amplifier to drive a load resistance of 5,000 ohms with an A_{vl} of -100 using small signal design (use specified V_{CQ}). $T_{min} = 10$ C, $T_{max} = 85$ C, $B_{min} = 100$, $B_{max} = 240$, $K_T = 1.2$, $K_B = 1.2$, $V_{CBmin} = 2$ volts. Do three designs: (1) $V_{CC} = 6$ volts, $R_C = 2,700$ ohms; (2) $V_{CC} = 12$ volts, $R_C = 4,700$ ohms; (3) $V_{CC} = 24$ volts, $R_C = 10,000$ ohms. Do analysis on each of your designs to verify that the required V_{CQ} is met and that A_{vl} is met.
4. Design a common-collector amplifier to drive a load resistance of 1,000 ohms using small signal design (let $V_{EQ} = V_{CC} - V_{CBmin} - V_{BE}$). Use $V_{CBmin} = 1$ volt and $V_{CEsat} = 0.1$ volts. Do three designs: (1) $V_{CC} = 6$ volts, $R_E = 1,500$ ohms; (2) $V_{CC} = 12$ volts, $R_E = 3,000$ ohms; (3) $V_{CC} = 24$ volts, $R_E = 7,500$ ohms. Do analysis on each of your designs to verify that the required V_{EQ} is met. Also calculate A_{vl} for each case.