

$P_{gain} = \frac{P_{out}}{P_{in}}$
 $dB = 10 \log_{10} \left(\frac{P_2}{P_1} \right)$

$I_D = I_S \left[e^{\frac{V_D}{nV_T}} - 1 \right]$
 $V_T = \frac{KT}{q} \quad \left| \begin{array}{l} K=1.38E-23 \\ \text{J/K} \\ T=K \\ q=1.602E-19 \end{array} \right.$

$r_d = \frac{V_T}{I_D} \quad \left| \begin{array}{l} V_T = 0.026 \\ @ 300K \end{array} \right.$

Power Supply Filter
 $C \approx \frac{24}{FR(\% \text{ ripple})}$
 half-wave (3% = 3)
 $C \approx \frac{8.6}{FR(\% \text{ ripple})}$
 full wave $f = \text{line freq}$
 $R = \frac{E_{load}}{I_{load}}$

BJT
 $I_C = \beta I_B = \left(\frac{\beta}{\beta+1} \right) I_E$
 $I_B = \frac{I_C}{\beta} = \frac{I_E}{\beta+1}$
 $I_E = (\beta+1) I_B = \left(\frac{\beta+1}{\beta} \right) I_C$


BJT Bias Anal.
 $I_E = \frac{V_{BB} - V_{BE} - V_{EE}}{R_E + \frac{R_B}{\beta+1}}$
 $V_C = V_{CC} - I_C R_C$
 $V_B = V_{BB} - I_B R_B$
 $V_E = V_{EE} + I_E R_E$
 $V_C > V_B > V_E$

BJT AC Anal.
 $r_e = \frac{V_T}{I_E}$
 $r_{ct} = \infty$
 $r_{bt} = (\beta+1)(r_e + R_E')$
 $r_{et} = r_e + \frac{R_B'}{\beta+1}$

CE: $R_{in} = R_B || r_{bt}$
 $R_o = R_C$
 $A_v = - \frac{\left(\frac{\beta}{\beta+1} \right) R_C}{r_e + R_E'}$

CC: $R_{in} = R_B || r_{bt}$
 $R_o = R_E || r_{et}$
 $A_v = \frac{R_E || R_L}{r_e + R_E || R_L}$

CB: $R_{in} = R_E || r_{et}$
 $R_o = R_C$
 $A_v = \left(\frac{\beta}{\beta+1} \right) \frac{R_C}{r_e}$

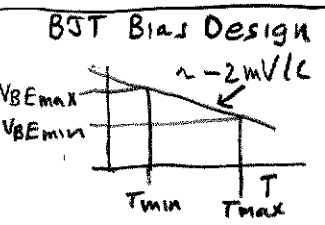

$K_T = \frac{I_{Cmax}}{I_{Cmin}}$
 $V_{BBmin} = K_T V_{BEmax} - V_{BEmin}$
 $K_T - 1$

$V_{BEnom} = \frac{V_{BEmax} + V_{BEmin}}{2}$
 $K_B = \frac{I_{Cmax}}{I_{Cmin}}$

$\left(\frac{R_B}{R_E} \right)_{max} = \frac{K_B \left[\frac{\beta_{max} + 1}{\beta_{max}} \right] - \left[\frac{\beta_{min} + 1}{\beta_{min}} \right]}{1 - \frac{K_B}{\beta_{min}}}$
 $B_{nom} = \sqrt{\beta_{min} \beta_{max}}$

CE (high gain case)
 $V_{CEopt} \approx \frac{2 \left(\frac{R_C}{R_L} \right) (V_{BB} + V_{CEmin}) + K V_{CE}}{2 \left(\frac{R_C}{R_L} \right) K}$
 $K \sim 0.2 \rightarrow 0.5$

CC
 $V_{CEopt} = \frac{(V_{CC} - V_{CEsat}) \left(1 + \frac{R_E}{R_L} \right)}{2 + \frac{R_E}{R_L}}$

$V_{BB} = (V_{CE} + V_{BE}) + V_{CE} \left(\frac{R_B}{R_E} \right)$
 $I_E = \frac{V_{BB} - V_{BE} - V_{EE}}{R_E \left(1 + \frac{R_B/R_E}{\beta+1} \right)}$

CE BJT AC gain
 $R_E' = \left(\frac{\beta}{\beta+1} \right) \left(\frac{R_C}{A_v} \right) - r_e$
 $R_E = \frac{R_E R_E'}{R_E - R_E'}$

JET
 $I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$
 $V_{GS} = V_P \left[1 - \sqrt{\frac{I_D}{I_{DSS}}} \right]$
 $g_m = 2 \sqrt{\frac{I_D I_{DSS}}{V_P}}$

Bias Anal. $R_S \neq 0$
 $V_K = V_{GG} - V_{SS} - V_P$
 $V_R = \frac{V_P^2}{I_{DSS}}$
 $X = \left| \frac{2 V_K R_S}{V_R} \right|$

$I_D = \left(\frac{V_R}{2 R_S^2} \right) \left[X + 1 - \sqrt{2X + 1} \right]$
 $V_D > (V_G - V_P)$
 $V_{DS} > (V_{GS} - V_P)$

$r_{dt} = \infty$
 $r_{gt} = \infty$
 $r_{st} = \frac{1}{g_m}$

CS:
 $R_{in} = R_G$
 $R_o = R_D$
 $A_v = \frac{-g_m R_D}{1 + g_m R_S}$

CD:
 $R_{in} = R_G$
 $R_o = R_S || \frac{1}{g_m}$
 $A_v = \frac{g_m R_S}{1 + g_m R_S}$

JFET BIAS DBS
 $V_{GS} = V_P \left[1 - \sqrt{\frac{I_D}{I_{DSS}}} \right]$
 $V_{GG} = V_{SS} + I_D R_S + V_{GS}$
 $R_S = \frac{V_{GG} - V_{GS} - V_{SS}}{I_D}$

Freq Response
 Low Cut off
 $f_c = \frac{1}{2\pi R_{series} C_{series}}$
 $f_{cnet} = \sqrt{f_{c1}^2 + f_{c2}^2 + f_{c3}^2}$

High Freq Cut off
 $f_c = \frac{1}{2\pi R_{shunt} C_{shunt}}$
 $f_{cnet} = \sqrt{\frac{1}{f_{c1}^2} + \frac{1}{f_{c2}^2} + \frac{1}{f_{c3}^2}}$

Cmiller
 $= C_A \left[|A_v| + 1 \right]$

Cascade Factors

| | |
|---|-------|
| 1 | 1 |
| 2 | 0.644 |
| 3 | 0.510 |
| 4 | 0.435 |
| 5 | 0.386 |
| 6 | 0.350 |