

$$P_{gain} = \frac{P_{out}}{P_{in}}, \text{ dB} = 10 \log_{10} \left(\frac{P_2}{P_1} \right)$$

Diodes

$$I_d = I_s [e^{(V_d/nV_T)} - 1]$$

$$V_T = \frac{kT}{q} \begin{cases} k = 1.38 \times 10^{-23} \text{ J/K} \\ T = K^\circ \\ q = 1.602 \times 10^{-19} \text{ C} \end{cases}$$

$$r_d = \frac{V_T}{I_d} \begin{cases} V_T = .026 \text{ V} \\ @ 300^\circ \text{K} \end{cases}$$

Power Supply Filter

$$\begin{cases} C \cong \frac{24}{FR(\% \text{ripple})} \\ \text{half-wave} (3\% = 3) \\ F = \text{line frequency} \end{cases}$$

$$\begin{cases} C \cong \frac{8.6}{FR(\% \text{ripple})} \\ \text{fullwave} \\ R = E_{load} / I_{load} \end{cases}$$

BJT Basics

$$I_C = \beta I_B = \left(\frac{\beta}{\beta + 1} \right) I_E$$

$$I_B = \frac{I_C}{\beta} = \frac{I_E}{\beta + 1}$$

$$I_E = (\beta + 1) I_B = \left(\frac{\beta + 1}{\beta} \right) I_C$$

$$I_E = \frac{V_{BB} - V_{BE} - V_{EE}}{R_E \left(1 + \frac{R_B/R_E}{(\beta + 1)} \right)}$$

$$V_{BB} = (V_{EQ} + V_{BE}) + \frac{V_{EQ}(R_B/R_E)}{(\beta + 1)}$$

BJT Bias Analysis

$$I_E = \frac{V_{BB} - V_{BE} - V_{EE}}{R_E + R_B/(\beta + 1)}$$

$$V_C = V_{CC} - I_C R_C$$

$$V_B = V_{BB} - I_B R_B$$

$$V_E = V_{EE} + I_E R_E$$

$$V_C > V_B > V_E$$

BJT AC Analysis

$$r_e = \frac{V_T}{I_E}$$

$$r_{ct} = \infty$$

$$r_{bt} = (\beta + 1)(r_e + R_E')$$

$$r_{et} = r_e + \frac{R_B'}{(\beta + 1)}$$

Common Emitter Analysis

$$R_{in} = R_E || r_{bt}$$

$$R_O = R_C$$

$$A_V = \frac{-[\beta/(\beta + 1)]R_C}{r_e + R_E'}$$

Common Collector Analysis

$$R_{in} = R_B || r_{bt}$$

$$R_O = R_E || r_{et}$$

$$A_{Vl} = \frac{R_E || R_L}{r_e + (R_E || R_L)}$$


Common Base Analysis

$$R_{in} = R_E || r_{et}$$

$$R_O = R_C$$

$$A_v = \frac{\beta R_C}{(\beta + 1) r_e}$$

BJT Bias Design

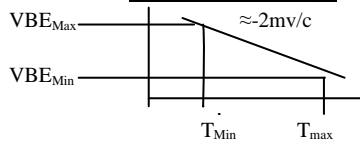

$$K_T = \frac{I_{CMax}}{I_{CMin}}$$

$$V_{BBmin} = \frac{K_T V_{BE Max} - V_{BE Min}}{K_T - 1}$$

$$V_{BE nom} = \frac{V_{BE Max} + V_{BE Min}}{2}$$

$$K_B = \frac{I_{C Max}}{I_{C Min}}$$

$$\left(\frac{R_B}{R_E} \right)_{Max} = \frac{K_B \left[\frac{\beta_{Max} + 1}{\beta_{Max}} \right] - \left[\frac{\beta_{Min} + 1}{\beta_{Min}} \right]}{\left[\frac{1}{\beta_{Min}} \right] - \left[\frac{K_B}{\beta_{Max}} \right]}$$

$$\beta_{Nom} = \sqrt{\beta_{Min} \cdot \beta_{Max}}$$

$$R_{B1} = R_B (V_{CC}/V_{BB})$$

$$R_{B2} = R_{B1} / [(V_{CC}/V_{BB}) - 1]$$

Common Emitter Design

(High Gain Case)

$$V_{CQopt} \cong \frac{2 \left(\frac{R_C}{R_L} \right) (V_{BB} + V_{CB Min}) + K(V_{CC})}{2 \left(\frac{R_C}{R_L} \right) K}$$

Where: $K \sim 0.2 \rightarrow 0.5$

(AC Gain)

$$R_E' = \left(\frac{\beta}{\beta + 1} \right) \left(\frac{R_C}{A_V} \right) - r_e$$

$$R_{E1} = \frac{R_E \cdot R_E'}{R_E - R_E'}$$

Common Collector Design

$$V_{EQ opt} = \frac{(V_{CC} - V_{CE Sat}) \left(1 + \frac{R_E}{R_L} \right)}{2 + (R_E/R_L)}$$

JFET Basics

$$I_D = I_{DSS} [1 - V_{GS}/V_P]^2$$

$$V_{GS} = V_P \left[1 - \sqrt{I_D/I_{DSS}} \right]$$

$$g_m = 2\sqrt{(I_D)(I_{DSS})}/V_P$$

Bias Analysis ($R_S \neq 0$)

$$V_K = V_{GG} - V_{SS} - V_P$$

$$V_R = V_P^2 / I_{DSS}$$

$$X = |2V_K R_S / V_R|$$

$$I_D = \left(\frac{V_R}{2R_S^2} \right) [X + 1 - \sqrt{2X + 1}]$$

$$V_D > (V_G - V_P), V_{DS} > (V_{GS} - V_P)$$

$$r_{dt} = \infty, r_{gt} = \infty, r_{st} = \frac{1}{g_m}$$

Common Source Analysis

$$R_{in} = R_G, \quad R_O = R_D$$

$$A_V = \frac{-g_m R_D}{1 + g_m R_S'}$$

Common Drain Analysis

$$R_{in} = R_G, \quad R_O = R_S || \frac{1}{g_m}$$

$$A_V = \frac{g_m R_S}{1 + g_m R_S}$$

JFET Bias Design

$$V_{GS} = V_P \left[1 - \sqrt{I_D/I_{DSS}} \right]$$

$$V_{GG} = V_{SS} + I_D R_S + V_{GS}$$

$$R_S = \frac{V_{GG} - V_{GS} - V_{SS}}{I_D}$$

Frequency Response Analysis

(Low Cutoff)

$$F_C = \frac{1}{2\pi R_{series} C_{series}}$$

$$F_{C net} = \sqrt{F_{c1}^2 + F_{c2}^2 + F_{c3}^2 + \dots}$$

(High Frequency Cutoff)

$$F_C = \frac{1}{2\pi R_{shunt} C_{shunt}}$$

$$F_{C net} = \frac{1}{\sqrt{\frac{1}{F_{c1}^2} + \frac{1}{F_{c2}^2} + \frac{1}{F_{c3}^2} + \dots}}$$

(Cascade Factor)

$$1 \quad 1$$

$$2 \quad 0.644$$

$$3 \quad 0.510$$

$$4 \quad 0.435$$

$$5 \quad 0.386$$

$$6 \quad 0.350$$

$$C_{Miller} = C_f [|A_V| + 1]$$