 


JFET Bias Analysis

by Kenneth A. Kuhn
Nov. 3, 2001, rev July 26, 2009

Introduction

The purpose of bias analysis is to determine the drain current of the JFET. Once the drain current is known then all other bias voltages can be calculated. The general circuit is shown in Figure 1. In many cases, the actual circuit will have only a single voltage source. Circuits can vary a bit so the first step is to transform whatever circuit is being analyzed into the form of Figure 1.



GENERAL JFET BIAS ANALYSIS

V_G , V_D , AND V_S ARE MEASURED
WITH RESPECT TO GROUND.

Figure 1: General JFET circuit for bias analysis

Development of the procedure

The basic equations written by inspection of Figure 1 are:

$$V_G = V_{GG} \text{ since we take } I_G \text{ to be } 0 \quad \text{Eq. 1}$$

$$V_S = V_{SS} + I_D * R_S \quad \text{Eq. 2}$$

$$V_D = V_{DD} - I_D * R_D \quad \text{Eq. 3}$$

JFET Bias Analysis

The drain current and the gate-source voltage are interrelated. If we know one then the other is easily calculated. The problem is that in Equations 1, 2, and 3 we know neither. The usual approach in solving this type of problem is to develop two different equations that represent the same variable related to the one we want to solve for. The equations are then set equal to each other which eliminates the related variable leaving just the desired variable in a single equation that we can solve. To determine I_D , we will substitute basic JFET terminal relationships into Equations 1, 2, and 3.

$$V_{GS} = V_G - V_S = V_{GG} - (V_{SS} + I_D * R_S) \quad \text{Eq. 4}$$

Substituting a basic JFET relationship for V_{GS} gives

$$V_{GS} = V_P * [1 - \sqrt{I_D/I_{DSS}}] = V_{GG} - V_{SS} - I_D * R_S \quad \text{Eq. 5}$$

It is now possible to solve Equation 5 for I_D

$$V_P * \sqrt{I_D/I_{DSS}} = V_{GG} - V_{SS} - V_P - I_D * R_S \quad \text{Eq. 6}$$

$$V_P^2 * I_D/I_{DSS} = (V_{GG} - V_{SS} - V_P - I_D * R_S)^2 \quad \text{Eq. 7}$$

It is obvious that expanding Equation 7 will be quite messy. Before proceeding it is useful to realize that the constant terms can be combined into simple constants.

$$\text{Let } V_K = V_{GG} - V_{SS} - V_P \quad \text{Eq. 8}$$

$$\text{Let } V_R = V_P^2/I_{DSS} \text{ which has units of voltage * resistance} \quad \text{Eq. 9}$$

Now Equation 7 can be written more simply as

$$V_R * I_D = (V_K - I_D * R_S)^2 \quad \text{Eq. 10}$$

Expanding Equation 10 produces the quadratic equation:

$$R_S^2 * I_D^2 - (2 * V_K * R_S + V_R) * I_D + V_K^2 = 0 \quad \text{Eq. 11}$$

Solving the quadratic equation for I_D gives:

$$I_D = \frac{2 * V_K * R_S + V_R \pm \sqrt{(2 * V_K * R_S + V_R)^2 - 4 * R_S^2 * V_K^2}}{2 * R_S^2} \quad \text{Eq. 12}$$

Equation 12 looks messy but there are some simplifications that can be done. Of the two possible solutions to Equation 12, only the negative root produces a valid I_D . Also, with the squaring and square root, some sign information is lost. We will have to adjust the sign of the result to agree with reality. Factoring out a common term produces:

JFET Bias Analysis

$$I_D = \frac{(V_R)}{(2 * R_S^2)} * \left[\frac{2 * V_K * R_S}{V_R} + 1 - \sqrt{\frac{4 * V_K * R_S}{V_R} + 1} \right] \quad \text{Eq. 13}$$

Equation 13 can be simplified further by making the following substitution:

$$X = \left| \frac{2 * V_K * R_S}{V_R} \right| \quad \text{Eq. 14}$$

The purpose of the absolute value signs is to make the calculation independent of whether an n-channel JFET or a p-channel JFET is being used as discussed below. Note that the numerator has units of voltage * resistance and that the denominator term has units of voltage * resistance as discussed earlier. Thus, Equation 14 has no dimension.

Substituting Equation 14 into Equation 13 gives:

$$I_D = \frac{(V_R)}{(2 * R_S^2)} * [X + 1 - \sqrt{2 * X + 1}] \quad \text{Eq. 15}$$

Equation 15 is the solution we have been seeking but there are some sign issues that must be dealt with. Note that V_R will be positive for n-channel JFETS and negative for p-channel JFETS. The constant, X , must be a positive number regardless of whether the JFET is N-channel or P-channel so we will use the absolute value of X . Now, looking at the expression inside the $[\]$ of Equation 15, it is obvious that that expression will always produce a positive result. Thus, for n-channel JFETS, I_D will be positive as it should and for p-channel JFETS, I_D will be negative as it should.

If R_S is 0 then Equation 15 will give the correct answer if a very small (say 0.01 Ohm) resistance is substituted for R_S . Or, in the special case when R_S is 0, one of the fundamental relations for the JFET can be used instead since the complexity of dealing with R_S is gone.

$$I_D = I_{DSS} * [1 - (V_{GS}/V_P)]^2 \quad \text{if } R_S \text{ is 0} \quad \text{Eq. 16}$$

JFET Bias Analysis

The sequence of steps to calculate the bias conditions is as follows:

1. Transform the actual circuit into the general form of Figure 1. The result of this is to establish: V_{DD} , V_{SS} , V_{GG} , R_D , R_S , and R_G .
2. Determine the I_{DSS} and V_P that will be used in the analysis. The analysis might be repeated for different values over the spread for a given JFET.
3. Use Equation 8 to calculate V_K if R_S is not zero
4. Use Equation 9 to calculate V_R if R_S is not zero
5. Use Equation 14 to calculate X if R_S is not zero
6. Use Equation 15 to calculate I_D if R_S is not zero
7. Or, use Equation 16 to calculate I_D if R_S is zero
8. Use Equation 1 to calculate V_G
9. Use Equation 2 to calculate V_S
10. Use Equation 3 to calculate V_D

The analysis is now complete but we must check to make sure that the JFET is operating in the active region. Otherwise, the JFET is not working per our model and our bias calculations are wrong.

The JFET is in the active region if

$$1. (V_D - V_S) > (V_G - V_S - V_P) \quad \text{Eq. 17}$$

which reduces to $V_D > (V_G - V_P)$ noting that V_P is negative for n-channel

and

$$2. 0 < [(V_G - V_S) / V_P] < 1 \quad V_{GS} \text{ must have the same sign as } V_P \quad \text{Eq. 18}$$

As a reality check,


$$3. 0 < I_D / I_{DSS} < 1 \quad I_D \text{ must have the same sign as } I_{DSS} \quad \text{Eq. 19}$$

A very common error is to use the wrong signs for I_{DSS} and V_P . The correct signs are as follows:


JFET type	Polarity of
	I_{DSS} V_P
N-channel	+ -
P-channel	- +

Figure 2 illustrates some common JFET circuits and the necessary transformations to be of the form in Figure 1.

JFET Bias Analysis

 

 
common circuit - already in standard form



$$R_G = R_{G3} + \underbrace{R_{G1} \parallel R_{G2}}$$

OFTEN NEGLIGIBLY
SMALL COMPARED TO R_{G3}

 
$$V_{GG} = V_{DD} * \frac{R_{G2}}{R_{G1} + R_{G2}}$$



$$R_G = R_{G3} + \underbrace{R_{G1} \parallel R_{G2}}$$

OFTEN NEGLIGIBLY
SMALL COMPARED TO R_{G3}
 
$$V_{GG} = V_{SS} * \frac{R_{G1}}{R_{G1} + R_{G2}}$$



$$R_D = R_{D1} \parallel R_{D2}$$

$$V_{DD} = V_{DD}' * \frac{R_{D2}}{R_{D1} + R_{D2}}$$

Figure 2: Common JFET circuits