

JFET Homework

Nov. 4, 2007, rev. Nov. 12, 2015

These homework problems provide practice with analysis and design involving the most common type of JFET circuits. There is one problem for each type of circuit. Answers are provided on the last page so the student can verify understanding. Note that some thought in addition to equations is required to solve some problems. All problems are based on a 2N3819 n-channel JFET. This is a very similar part (except for different pin outs you probably could not tell them apart) to the MPF102 used in lab. Summary specifications are below. One way to know for sure that what you are doing with these problems is right is to build some sample circuits in lab. Nothing beats hands-on experience.

Summary 2N3819 Specifications

| | <u>Min</u> | <u>Typ.</u> | <u>Max</u> | <u>Unit</u> |
|-----------|------------|-------------|------------|-------------|
| I_{DSS} | 2 | 10 | 20 | mA |
| V_P | -0.9 | -3 | -8 | Volts |

Notes:

A_v = unloaded voltage gain.


A_{v_l} = loaded voltage gain.

Assume voltage divider for V_{GG} has negligibly small resistance compared to R_G .

Use standard resistor values.

Analysis problems

 1. Analyze the following circuit for operation at the low, typical, and high values of the JFET specifications. Determine I_D , V_{GS} , V_D , V_G , V_S , g_m , A_v , A_{v_l} , and power gain in dB.




$V_{DD} = 20$ volts, $R_D = 680$, $R_L = 470$, $R_G = 1M$, $R_S = 100$, $R_{S1} = 22$

JFET Homework

Answers for Min, Typ, and Max

| <u>ID</u> | <u>VGS</u> | <u>VD</u> | <u>VG</u> | <u>VS</u> | <u>gm</u> | <u>Av</u> | <u>Avl</u> | <u>Pg (dB)</u> |
|-----------|------------|-----------|-----------|-----------|-----------|-----------|------------|----------------|
| 0.00142 | -0.142 | 19.04 | 0.00 | 0.14 | 0.00374 | -2.385 | -0.975 | 33.056 |
| 0.00626 | -0.626 | 15.74 | 0.00 | 0.63 | 0.00528 | -3.276 | -1.339 | 35.813 |
| 0.01373 | -1.373 | 10.67 | 0.00 | 1.37 | 0.00414 | -2.621 | -1.071 | 33.876 |

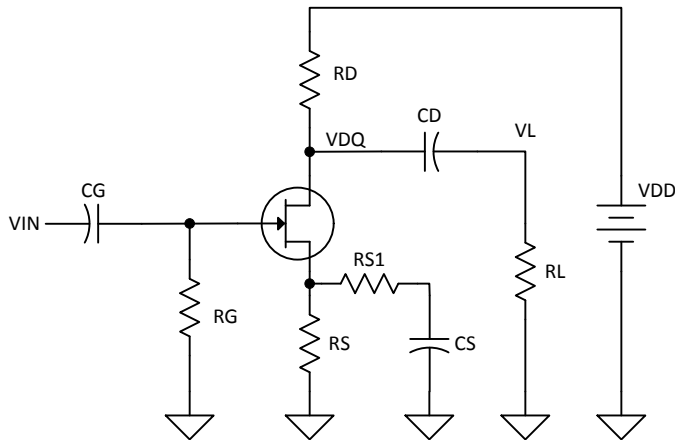2. Analyze the following circuit for operation at the low, typical, and high values of the JFET specifications. Determine I_D , V_{GS} , V_D , V_G , V_S , g_m , A_v , A_{vL} , and power gain in dB. This is a different way of implementing problem 1. Note how the characteristics are more stable with device variation than in the first problem.




$V_{DD} = 20$ volts, $R_D = 680$, $R_L = 470$, $R_G = 1M$, $R_S = 1.8$ K, $R_{S1} = 22$
 $R_A = 75$ K, $R_B = 10$ K.

Answers for Min, Typ, and Max

| <u>ID</u> | <u>VGS</u> | <u>VD</u> | <u>VG</u> | <u>VS</u> | <u>gm</u> | <u>Av</u> | <u>Avl</u> | <u>Pg (dB)</u> |
|-----------|------------|-----------|-----------|-----------|-----------|-----------|------------|----------------|
| 0.00139 | -0.150 | 19.05 | 2.35 | 2.50 | 0.00371 | -2.332 | -0.953 | 32.862 |
| 0.00219 | -1.595 | 18.51 | 2.35 | 3.95 | 0.00312 | -1.988 | -0.813 | 31.476 |
| 0.00381 | -4.508 | 17.41 | 2.35 | 6.86 | 0.00218 | -1.417 | -0.579 | 28.535 |

JFET Homework

 3. Analyze the following circuit for operation at the low, typical, and high values of the JFET specifications. Determine I_D , V_{GS} , V_D , V_G , V_S , g_m , A_v , A_{vL} , and power gain in dB. See problem 5 for an improved version of this circuit.




$V_{DD} = 20V$, $R_S = 100 \text{ Ohms}$, $R_L = 470 \text{ Ohms}$, $R_G = 1 \text{ M}$.

Answers for Min, Typ, and Max

| <u>ID</u> | <u>VGS</u> | <u>VD</u> | <u>VG</u> | <u>VS</u> | <u>gm</u> | <u>Av</u> | <u>AvL</u> | <u>Pg (dB)</u> |
|-----------|------------|-----------|-----------|-----------|-----------|-----------|------------|----------------|
| 0.00142 | -0.142 | 20.00 | 0.00 | 0.14 | 0.00374 | 0.272 | 0.236 | 20.733 |
| 0.00626 | -0.626 | 20.00 | 0.00 | 0.63 | 0.00528 | 0.345 | 0.303 | 22.911 |
| 0.01373 | -1.373 | 20.00 | 0.00 | 1.37 | 0.00414 | 0.293 | 0.255 | 21.396 |

 4. Analyze the following circuit for operation at the low, typical, and high values of the JFET specifications. Determine I_D , V_{GS} , V_D , V_G , V_S , g_m , A_v , A_{vL} , and power gain in dB. Observe that this is similar to problem 2 except that the circuit is even more stable because of the larger voltage drop across R_S – i.e. more like a constant current.




JFET Homework

$V_{DD} = 20V$, $V_{SS} = -2.5V$, $R_S = 1.8K$, $R_D = 680\ \Omega$, $R_L = 470\ \Omega$, $R_G = 1M$, $R_{S1} = 22\ \Omega$.

Answers for Min, Typ, and Max

| <u>ID</u> | <u>VGS</u> | <u>VD</u> | <u>VG</u> | <u>VS</u> | <u>gm</u> | <u>Av</u> | <u>Avl</u> | <u>Pg (dB)</u> |
|-----------|------------|-----------|-----------|-----------|-----------|-----------|------------|----------------|
| 0.00146 | -0.131 | 19.01 | 0.00 | 0.13 | 0.00380 | -2.386 | -0.975 | 33.062 |
| 0.00226 | -1.573 | 18.46 | 0.00 | 1.57 | 0.00317 | -2.017 | -0.824 | 31.603 |
| 0.00388 | -4.478 | 17.36 | 0.00 | 4.48 | 0.00220 | -1.429 | -0.584 | 28.605 |

 5. Analyze the following circuit for operation at the low, typical, and high values of the JFET specifications. Determine I_D , V_{GS} , V_D , V_G , V_S , g_m , A_v , A_{v1} , and power gain in dB. Observe that this circuit is more stable and works better than in problem 3



$V_{DD} = 20V$, $R_S = 2.4K$, $R_L = 470\ \Omega$, $R_G = 1M$, $R_A = 51K$, $R_B = 10K$.

Answers for Min, Typ, and Max


| <u>ID</u> | <u>VGS</u> | <u>VD</u> | <u>VG</u> | <u>VS</u> | <u>gm</u> | <u>Av</u> | <u>Avl</u> | <u>Pg (dB)</u> |
|-----------|------------|-----------|-----------|-----------|-----------|-----------|------------|----------------|
| 0.00142 | -0.140 | 20.00 | 3.28 | 3.42 | 0.00375 | 0.900 | 0.596 | 28.782 |
| 0.00205 | -1.642 | 20.00 | 3.28 | 4.92 | 0.00302 | 0.879 | 0.543 | 27.969 |
| 0.00334 | -4.732 | 20.00 | 3.28 | 8.01 | 0.00204 | 0.831 | 0.445 | 26.252 |

JFET Homework


Design Problems

These problems are identical to problems 1 – 5 except approached from the design perspective – see problems 1-5 for the answers. The result is the designs you analyzed in the earlier problems. In all cases use the V_P data for the minimum I_{DSS} .

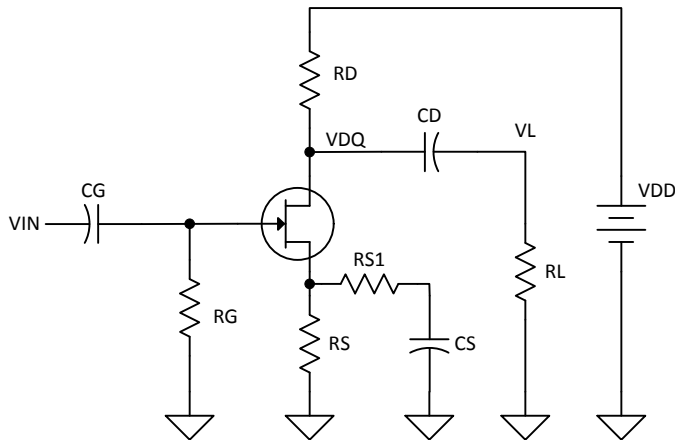6. Complete the design of the following circuit. V_{DD} is +20 volts. The input resistance is to be 1 M. The drain current is to be 70% of I_{DSSmin} . The load resistor is 470 Ohms and R_D is 680 Ohms. A_v is to be -2.4 for a minimum I_{DSS} unit. Determine R_S and R_{S1} .




 7. Complete the design of the following circuit. V_{DD} is +20 volts. The input resistance is to be 1 M. The drain current is to be 70% of I_{DSSmin} . The load resistor is 470 Ohms, R^S is 1.8K and R_D is 680 Ohms. A_v is to be -2.3 for a minimum I_{DSS} unit. Determine the required V_{GG} at the voltage divider formed by R_A and R_B (10K). Determine R_{S1} and R_A .




JFET Homework

 8. Complete the design of the following circuit. V_{DD} is +20 volts. The input resistance is to be 1 M. The drain current is to be 70% of I_{DSSmin} . The load resistor is 470 Ohms. Determine R_S . Remember that problem 3 is the analysis of this.



 9. Complete the design of the following circuit. V_{DD} is +20 volts and V_{SS} is -2.5 volts. The input resistance is to be 1 M. The drain current is to be 70% of I_{DSSmin} . The load resistor is 470 Ohms and R_D is 680 Ohms. V_S is to be close to as high as possible consistent with using an FET with the maximum V_P value (hint: reverse engineer problem 4 – think in terms of needing a V_{DS} of at least 8 volts). A_v is to be -2.4 for a minimum I_{DSS} unit. Determine R_S and R_{S1} . Remember that problem 4 is an analysis of this.



JFET Homework

10. Complete the design of the following circuit. V_{DD} is +20 volts. The input resistance is to be 1 M. The drain current is to be 70% of I_{DSSmin} . The load resistor is 470 Ohms. V_S is to be as high as possible consistent with using an FET with the maximum V_P value (hint: reverse engineer problem 5 – think in terms of needing a V_{DS} of at least 8 volts). Determine the required V_{GG} at the voltage divider formed by R_A and R_B (10K). Determine R_S and R_{S1} and R_A .

