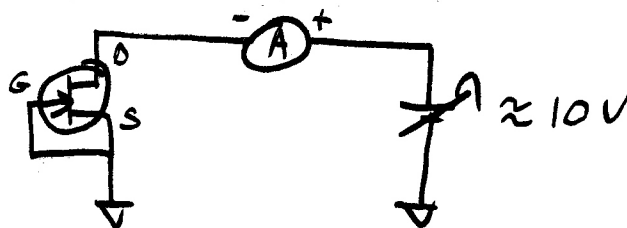


DETERMINING I_{DSS} AND V_P OF A JFET

K. KUHN
9-28-03


THE METHOD SHOWN IS FOR AN N-CHANNEL JFET, SIMPLY REVERSE POLARITIES FOR A P-CHANNEL JFET.

- ① MEASURE I_{DSS} USING THE FOLLOWING CIRCUIT



READ THE CURRENT ON THE AMMETER - THIS IS I_{DSS} . IF THE APPLIED VOLTAGE IS INCREASED BY SEVERAL VOLTS THE AMMETER SHOULD INCREASE BY ONLY A SMALL AMOUNT - PERHAPS $\approx 100 \mu A$.

- ② CONNECT THE FOLLOWING CIRCUIT

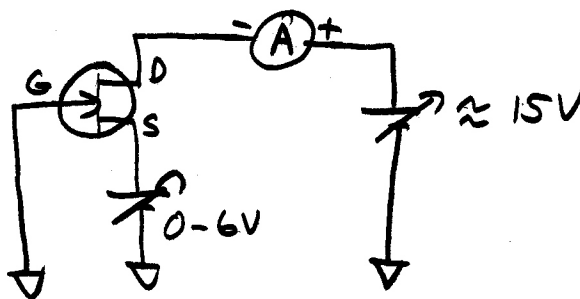

ADJUST THE 0-6 VOLT SUPPLY UNTIL THE AMMETER READS $\frac{1}{4} I_{DSS}$. MEASURE THE VOLTAGE OF THE 0-6 VOLT SUPPLY AND MULTIPLY BY -2. THIS IS ROUGHLY V_P .

VP IS HARD TO DIRECTLY MEASURE SINCE THE DRAIN CURRENT NEVER REACHES EXACTLY ZERO AND IT IS A BIT SUBJECTIVE AS TO WHERE THE CURRENT IS PRACTICALLY ZERO. THE METHOD USED HERE USES TWO EASY MEASUREMENTS AND PROJECTS WHERE VP IS WITH OUR STANDARD MODEL. THUS, THIS METHOD PRODUCES A VP THAT SHOULD GIVE ACCURATE RESULTS WITH OUR MODEL. HERE IS THE DERIVATION.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$K I_{DSS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$K = \frac{I_D @ V_{GS} < 0}{I_{DSS} @ V_{GS} = 0}$$

$$K = 1 - 2 \frac{V_{GS}}{V_P} + \frac{V_{GS}^2}{V_P^2}$$

$$K V_P^2 = V_P^2 - 2 V_{GS} V_P + V_{GS}^2$$

$$(1-K) V_P^2 - 2 V_{GS} V_P + V_{GS}^2 = 0$$

$$V_P = \frac{2 V_{GS} \pm \sqrt{4 V_{GS}^2 - 4(1-K) V_{GS}^2}}{2(1-K)}$$

WHICH REDUCES TO

$$V_P = V_{GS} \left[\frac{1 + \sqrt{K}}{1-K} \right]$$

IF $K = 0.25$ THEN $V_P = 2 V_{GS}$ THAT MAKES $I_D = I_{DSS}/4$. WILL WORK FOR ANY GOOD VALUE OF K . BUT $K = 0.25$ IS EASY.