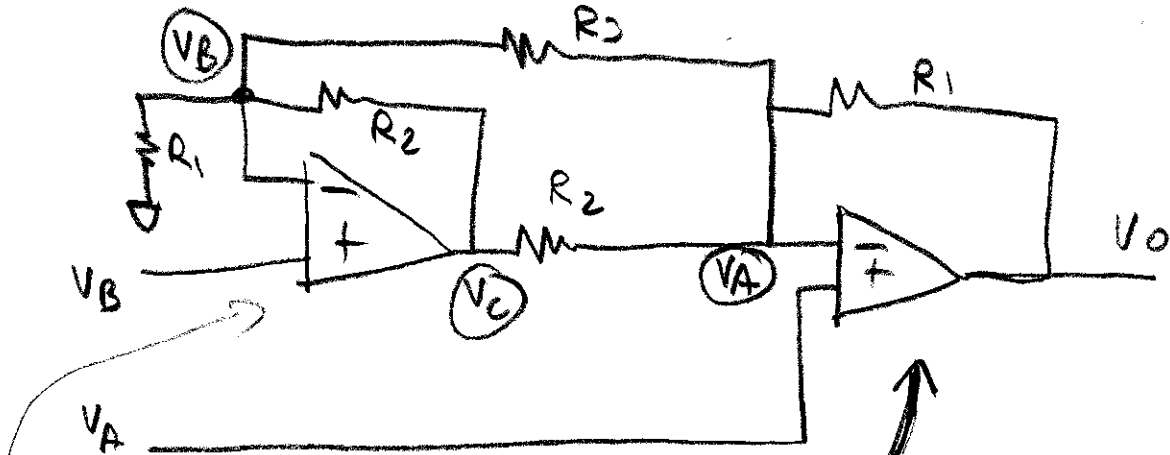


# TWO OP-AMP DIFFERENCE CIRCUIT

K. KUAN  
2-15-93



$$\left. \begin{aligned} \frac{V_C - V_A}{R_2} + \frac{V_B - V_A}{R_3} + \frac{V_O - V_A}{R_1} &= 0 \\ \frac{V_A - V_B}{R_2} + \frac{0 - V_B}{R_1} + \frac{V_C - V_B}{R_2} &= 0 \end{aligned} \right\} \begin{array}{l} \text{THIS IS} \\ \text{THE LONG} \\ \text{WAY - BUT} \\ \text{IT WORKS} \end{array}$$

$$\begin{aligned} R_1 R_3 V_C - R_1 R_3 V_A + R_1 R_2 V_B - R_1 R_2 V_A + R_2 R_3 V_O - R_2 R_3 V_A &= 0 \\ R_1 R_2 V_A - R_1 R_2 V_B - R_2 R_3 V_B + R_1 R_3 V_C - R_1 R_3 V_B &= 0 \end{aligned}$$

$$V_O = \left[ (R_1 R_2 + R_1 R_3 + R_2 R_3) V_A - R_1 R_2 V_B - R_1 R_3 V_C \right] / R_2 R_3$$

$$V_C = \left[ (R_1 R_2 + R_1 R_3 + R_2 R_3) V_B - R_1 R_2 V_A \right] / R_1 R_3$$

$$V_O = \frac{(R_1 R_2 + R_1 R_3 + R_2 R_3) V_A - R_1 R_2 V_B - (R_1 R_2 + R_1 R_3 + R_2 R_3) V_B + R_1 R_2 V_A}{R_2 R_3}$$


$$V_O = (V_A - V_B) \left[ \frac{2R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2 R_3} \right]$$

$$V_O = (V_A - V_B) \left[ 1 + \frac{R_1}{R_2} + \frac{2R_1}{R_3} \right]$$

# ANALYSIS/DESIGN PROBLEM

12/31/97  
K. KUHN

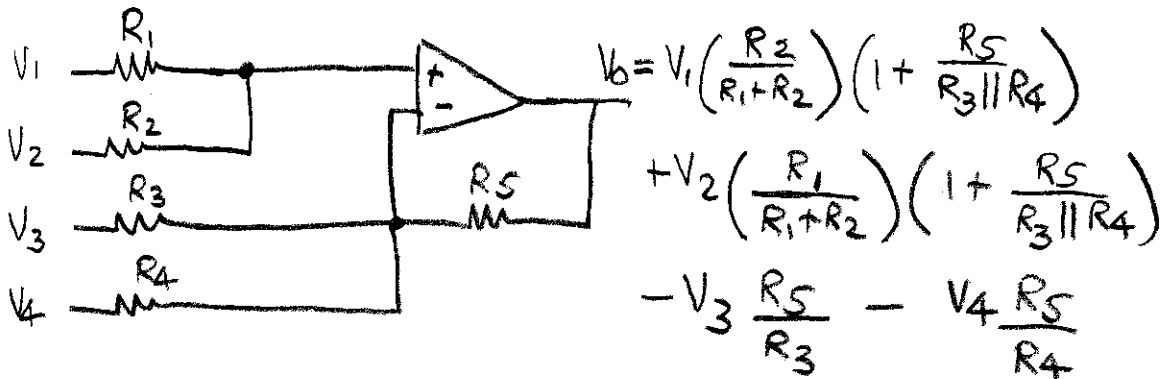1. DERIVE THE TRANSFER FUNCTION GIVEN FOR THE FOLLOWING CIRCUIT.



$$V_0 = V_1 \left( \frac{R_2}{R_1 + R_2} \right) \left( 1 + \frac{R_5}{R_3 \parallel R_4} \right)$$

$$+ V_2 \left( \frac{R_1}{R_1 + R_2} \right) \left( 1 + \frac{R_5}{R_3 \parallel R_4} \right)$$

$$- V_3 \frac{R_5}{R_3} - V_4 \frac{R_5}{R_4}$$

2. DETERMINE A SET OF RESISTORS TO IMPLEMENT THE FOLLOWING TRANSFER FUNCTION:

$$V_0 = 2.85V_1 + 2.19V_2 - 2.40V_3 - 1.64V_4$$

DERIVE THE DESIGN EQUATIONS FOR THIS CIRCUIT, USE RATIOS TO ELIMINATE UNNECESSARY VARIABLES. I.E.

CHOOSE  $R_1$ , THEN  $R_2 = K_1 R_1$  } WHY DOES THIS PARTICULAR CHOICE  
 CHOOSE  $R_3$ , THEN  $R_4 = K_2 R_3$  } SIMPLIFY THINGS?

ALSO, REPRESENT THE TRANSFER FUNCTION AS

$$V_0 = G_1 V_1 + G_2 V_2 - G_3 V_3 - G_4 V_4$$

NOW THE TRANSFER EQUATION CAN BE SOLVED FOR  $K_1$ ,  $K_2$ , AND  $R_5$ . FROM  $K_1$  AND  $K_2$  WE OBTAIN  $R_2$  AND  $R_4$ .


ONE SOLUTION:

$$R_1 = 10k, R_2 = 13k, R_3 = 15k, R_4 = 22k, R_5 = 36k$$
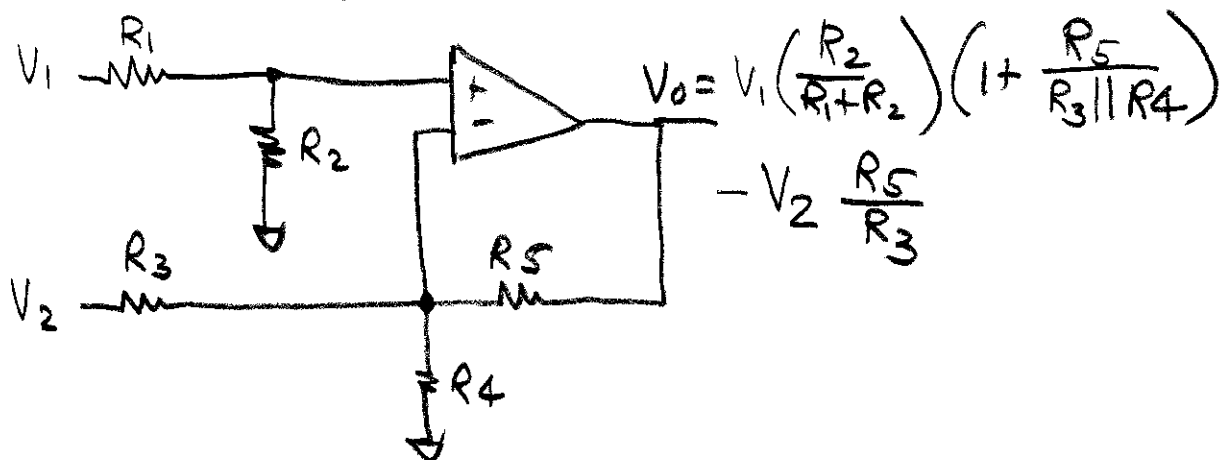
## GENERAL DIFFERENCE CIRCUIT

12 31 97  
K. KUHN

DERIVE THE TRANSFER FUNCTION GIVEN FOR THE FOLLOWING CIRCUIT.



DERIVE THE DESIGN EQUATIONS FOR THIS CIRCUIT

GIVEN:  $V_0 = G_1 V_1 - G_2 V_2$ , FIND  $R_1, R_2, R_3, R_4, R_5$

NOTE: DEPENDING ON VALUES FOR  $G_1$  +  $G_2$  IT IS POSSIBLE FOR EITHER  $R_2$  OR  $R_4$  TO BE INFINITE (I.E. NOT NEEDED).

USE  $R_1 = R_3 = 10K$  AND DETERMINE  $R_2, R_4, R_5$  FOR

$$V_0 = 10V_1 - V_2$$

$$V_0 = 5V_1 - 2V_2$$

$$V_0 = 3V_1 - 3V_2$$

$$V_0 = 2V_1 - 5V_2$$

$$V_0 = V_1 - 10V_2$$

CHECK EACH RESULT BY SUBSTITUTING INTO THE GENERAL TRANSFER FUNCTION ABOVE.