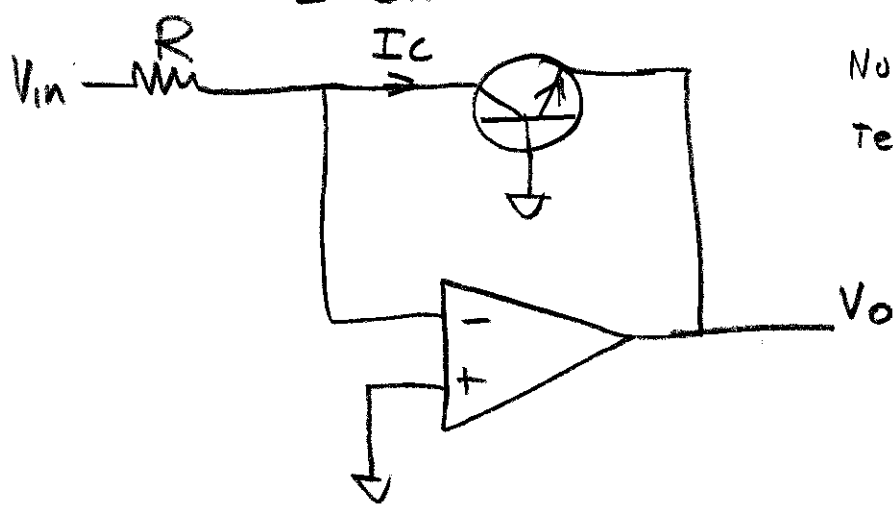


LOGARITHMIC CIRCUIT



Note: NPN circuit
text is for PNP

FROM EBERS-MOLL EQUATIONS:

$$I_c = C_{21} (e^{V_{EB}/(KT/q)} - 1) + C_{22} (e^{V_{CB}/(KT/q)} - 1)$$

T IS TEMPERATURE IN DEGREE KELVIN

q IS ELECTRON CHARGE = 1.6×10^{-19} COULOMBS

k IS BOLTSMANN'S CONSTANT = 1.38×10^{-23} JOULES/OK

THUS KT/q IS IN UNITS OF JOULES/COULOMB OR VOLTS

NOTE: $V_{EB} = -V_o$.

$V_{CB} = 0$ SO ONLY FIRST TERM OF I_c EQN IS USED

THUS: $I_c = C_{21} (e^{-V_o/(KT/q)} - 1)$ WHICH CAN BE

WRITTEN AS: $I_c + C_{21} = C_{21} (e^{-V_o/(KT/q)})$

SINCE C_{21} IS TYPICALLY IN THE FEMTO-AMPERE RANGE (10^{-15}) AND I_c IS TYPICALLY BETWEEN 1uA AND 10mA, WE CAN WRITE:

$$I_c = C_{21} (e^{-V_o/(KT/q)})$$

NOTE ALSO THAT $I_C = V_{in}/R$. SO;

$$C_{21} e^{-V_0/KT/q} = \frac{V_{in}}{R}$$

DIVIDING BY C_{21} AND TAKING LN:


$$\frac{-V_0}{KT/q} = \ln\left(\frac{V_{in}}{C_{21} R}\right) = \ln\frac{V_{in}}{R} - \ln C_{21}$$

THUS:

$$V_0 = -\frac{KT}{q} \left[\ln\frac{V_{in}}{R} - \ln C_{21} \right]$$

IMPROVED CIRCUIT

Q_1, Q_2 matched

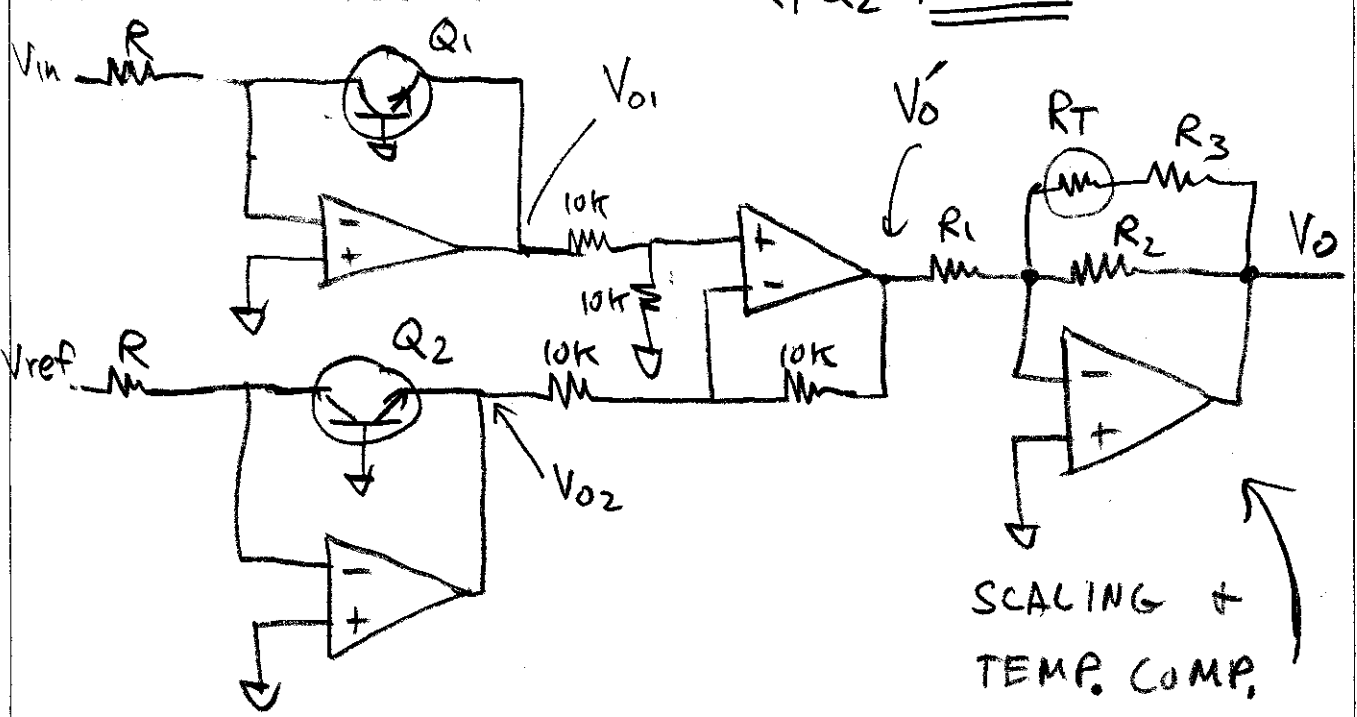

$$V_{01} = -\frac{KT}{q} \left[\ln\left(\frac{V_{in}}{R}\right) - \ln C_{21} \right]$$

$$V_{02} = -\frac{KT}{q} \left[\ln\left(\frac{V_{ref}}{R}\right) - \ln C_{21} \right]$$

$$V_0' = -\frac{kT}{q} \left[\ln\left(\frac{V_{in}}{R}\right) - \ln C_{21} - \ln\left(\frac{V_{ref}}{R}\right) + \ln C_{21} \right]$$

$$V_0' = -\frac{kT}{q} \left[\ln\left(\frac{V_{in}}{R}\right) - \ln\left(\frac{V_{ref}}{R}\right) \right]$$

$$V_0' = -\frac{kT}{q} \left[\ln\left(\frac{V_{in}}{V_{ref}}\right) \right]$$

NOTE:

1. C_{21} TERM CANCELS IF Q_1, Q_2 MATCHED
2. NOTE SENSITIVITY TO TEMPERATURE

FINAL IMPROVEMENT:

1. ADD SCALING TO PRODUCE DESIRED LOG FUNCTION.
2. USE R_T (THERMISTOR — RESISTANCE DECREASES WITH INCREASE IN TEMP.) SUCH THAT SCALING GAIN DECREASES AT THE RIGHT RATE WITH TEMPERATURE INCREASE TO GREATLY REDUCE SENSITIVITY TO TEMPERATURE.