

Frequency Filter Notes

Ken Kuhn hand notes

Contents:

Butterworth Low-pass Filter Notes

Chebyshev Low-pass Filter Notes

Sallen-Key Circuits – second order, analysis / design

Non-inverting low-pass filter

Inverting low-pass filter

Non-inverting high-pass filter

Inverting high-pass filter

Non-inverting bandpass filter

Inverting bandpass filter and design note

Biquad Filter Analysis

BUTTERWORTH LOW-PASS FILTER

K. KUHN
JAN 30, 04

1/5

THE NORMALIZED RESPONSE OF THE FILTER
IS GIVEN BY

$$R = \left| \frac{A_{vf}}{A_{v0}} \right| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_c} \right)^{2n}}}$$


f = FREQUENCY OF INTEREST

f_c = CUTOFF FREQUENCY ($R = \frac{1}{\sqrt{2}} = .707$)

A_{vf} = RESPONSE AT FREQUENCY, f

A_{v0} = RESPONSE AT DC (TYPICALLY 1.0)

n = FILTER ORDER ($n = 1, 2, 3, \dots$)

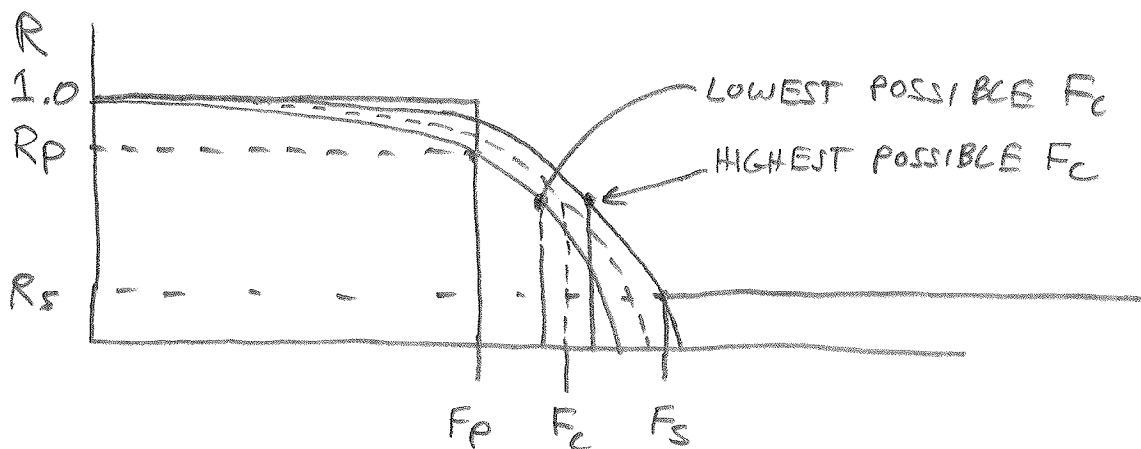

R_p = SMALLEST ALLOWABLE RESPONSE IN PASSBAND
 R_p TYPICALLY IN THE RANGE 0.75 TO 0.95

R_s = LARGEST ALLOWABLE RESPONSE IN STOPBAND
 R_s TYPICALLY LESS THAN 0.03

F_p = HIGHEST FREQUENCY IN PASSBAND

F_s = LOWEST FREQUENCY IN STOPBAND

$$F_c = \text{CUTOFF FREQUENCY} \quad R = \frac{1}{\sqrt{2}} = .707$$

F_c IS GENERALLY THE AVERAGE OF THE LOWEST POSSIBLE F_{cL} THAT JUST MEETS THE PASSBAND SPEC AND THE HIGHEST POSSIBLE F_{cH} THAT JUST MEETS THE STOPBAND SPEC. THE TWO CUTOFF FREQUENCIES ARISE BECAUSE OF INTEGER ROUNDING IN THE COMPUTATION OF n .

THE DESIGN PROBLEM IS:

GIVEN: R_p, R_s, F_p, F_s

FIND: n, F_c

$$R_s = \frac{1}{\sqrt{1 + \left(\frac{F_s}{F_c}\right)^{2n}}}$$

$$R_p = \frac{1}{\sqrt{1 + \left(\frac{F_p}{F_c}\right)^{2n}}}$$

SOLVE FOR n, F_c

$$\left. \begin{aligned} R_s^2 &= \frac{1}{1 + \left(\frac{F_s}{F_c}\right)^{2n}} \\ R_p^2 &= \frac{1}{1 + \left(\frac{F_p}{F_c}\right)^{2n}} \end{aligned} \right\}$$

BASIC SET OF EQUATIONS

WE FIRST SOLVE FOR n
THEN FOR F_c

$$\left(\frac{F_s}{F_c}\right)^{2n} = \frac{1}{R_s^2} - 1$$

$$\left(\frac{F_p}{F_c}\right)^{2n} = \frac{1}{R_p^2} - 1$$

$$\left(\frac{F_s}{F_p}\right)^{2n} = \frac{\frac{1}{R_s^2} - 1}{\frac{1}{R_p^2} - 1}$$

$$2n \ln\left(\frac{F_s}{F_p}\right) = \ln\left(\frac{\frac{1}{R_s^2} - 1}{\frac{1}{R_p^2} - 1}\right)$$

$$n = \frac{\ln\left(\frac{\frac{1}{R_s^2} - 1}{\frac{1}{R_p^2} - 1}\right)}{2 \ln\left(\frac{F_s}{F_p}\right)}$$

$$n = \text{integer}(n+1)$$

Round n up to next integer

THE LOWEST POSSIBLE CUTOFF FREQUENCY IS FOUND BY SOLVING:

$$R_p = \frac{1}{\sqrt{1 + \left(\frac{F_p}{F_{CL}}\right)^{2n}}} \quad \text{FOR } F_{CL}$$

$$1 + \left(\frac{F_p}{F_{CL}}\right)^{2n} = \frac{1}{R_p^2}$$

$$2n \ln\left(\frac{F_p}{F_{CL}}\right) = \ln\left(\frac{1}{R_p^2} - 1\right)$$

$$\frac{F_p}{F_{CL}} = e^{\left[\ln\left(\frac{1}{R_p^2} - 1\right)/2n\right]}$$

$$F_{CL} = \frac{F_p}{e^{\left[\ln\left(\frac{1}{R_p^2} - 1\right)/2n\right]}}$$


THE HIGHEST POSSIBLE CUTOFF FREQUENCY IS FOUND BY SOLVING

$$R_s = \frac{1}{\sqrt{1 + \left(\frac{F_s}{F_{CH}}\right)^{2n}}} \quad \text{FOR } F_{CH}$$

$$F_{CH} = \frac{F_s}{e^{\left[\ln\left(\frac{1}{R_s^2} - 1\right)/2n\right]}}$$

$$F_c = \frac{(F_{CL} + F_{CH})}{2}$$


THE BUTTERWORTH POLE LOCATIONS ARE

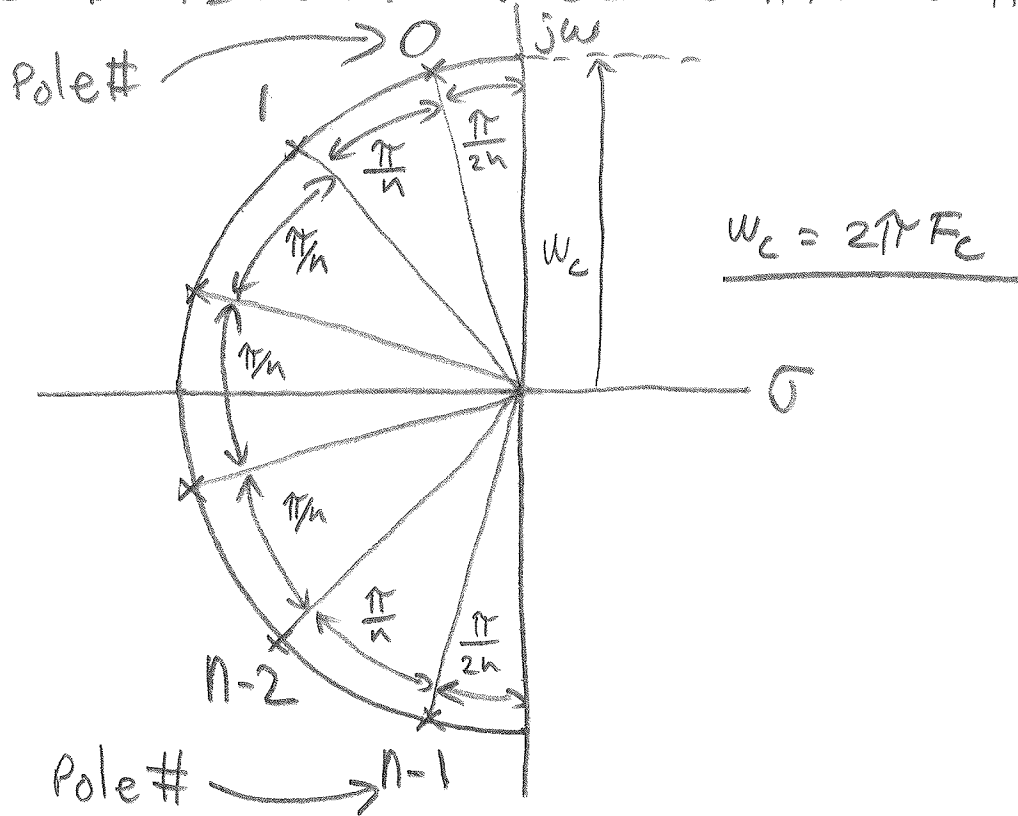

$$\begin{aligned} \sigma_k &= w_c \cos\left(\frac{\pi}{2} \left(1 + \frac{(2k+1)}{n}\right)\right) \\ \omega_k &= w_c \sin\left(\frac{\pi}{2} \left(1 + \frac{(2k+1)}{n}\right)\right) \end{aligned} \quad \left. \vphantom{\begin{aligned} \sigma_k &= w_c \cos\left(\frac{\pi}{2} \left(1 + \frac{(2k+1)}{n}\right)\right) \\ \omega_k &= w_c \sin\left(\frac{\pi}{2} \left(1 + \frac{(2k+1)}{n}\right)\right) \right\} k = 0, 1, \dots, n-1$$

CHEBYSHEV LOW PASS FILTER

Jan 26, 98
K. KUHN

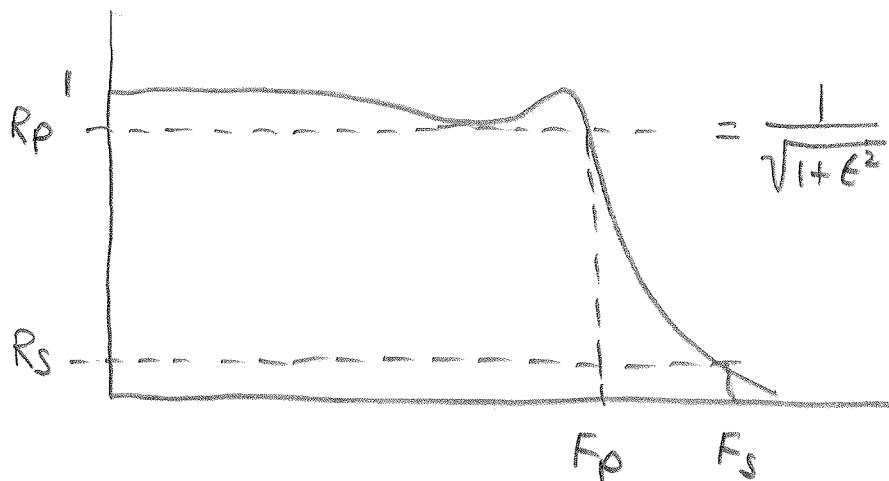

$$\textcircled{1} \quad \epsilon = \sqrt{\frac{1}{R_p^2} - 1}$$


$$\textcircled{2} \quad n = \frac{\cosh^{-1} \left[\sqrt{\left(\frac{1}{R_s^2} - 1 \right)} / \epsilon \right]}{\cosh^{-1} (F_s / F_p)}$$

Round n up to next higher integer

$$\begin{aligned} \text{pole}(k) = & \omega_p \cos \left[\frac{\pi}{2} \left(1 + \frac{2k+1}{n} \right) \right] \sinh \left(\frac{1}{n} \sinh^{-1} \left(\frac{1}{\epsilon} \right) \right) \\ & \pm j \omega_p \sin \left[\frac{\pi}{2} \left(1 + \frac{2k+1}{n} \right) \right] \cosh \left(\frac{1}{n} \sinh^{-1} \left(\frac{1}{\epsilon} \right) \right) \end{aligned}$$

for $k = 0, 1, 2, \dots, n-1$
Save time using symmetry!

Poles located on ellipse

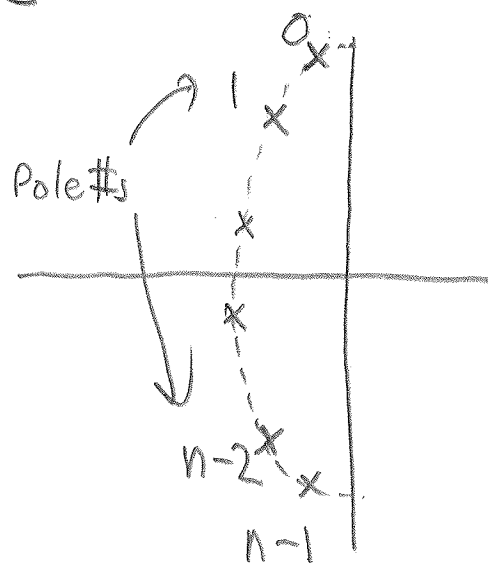


Sallen-Key Unity Gain Low-Pass Filter

1 of 2

June 4, 1998

K. Kuhn

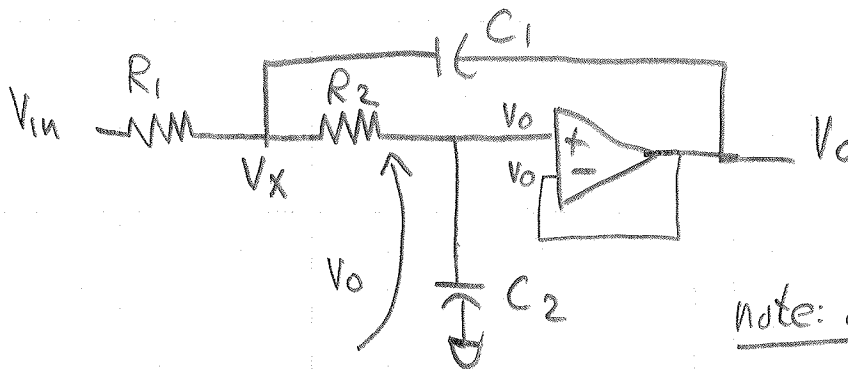

note: all V's are V'(s)

$$\frac{V_{in} - V_x}{R_1} = \frac{V_x - V_o}{R_2} + \frac{V_x - V_o}{1/C_1 s}$$

$$R_2(V_{in} - V_x) = R_1(V_x - V_o) + R_1 R_2 C_1 s(V_x - V_o)$$

$$V_o = \frac{V_x}{R_2 C_2 s + 1} \quad \therefore V_x = V_o(R_2 C_2 s + 1)$$

$$R_2(V_{in} - V_o(R_2 C_2 s + 1)) = R_1 V_o(R_2 C_2 s) + R_1 R_2 C_1 V_o(R_2 C_2 s)$$

$$V_o(R_1 C_2 s + R_1 C_1 R_2 C_2 s^2 + R_2 C_2 s + 1) = V_{in}$$

$$\frac{V_o(s)}{V_{in}(s)} = \frac{1}{R_1 C_1 R_2 C_2 s^2 + (R_1 + R_2) C_2 s + 1}$$

$$= \frac{1/R_1 C_1 R_2 C_2}{s^2 + \frac{R_1 + R_2}{R_1 R_2 C_1} s + \frac{1}{R_1 C_1 R_2 C_2}}$$

$$= \frac{\omega_n^2}{s^2 + 2 \zeta \omega_n s + \omega_n^2}$$

$$w_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$2 \zeta w_n = \frac{R_1 + R_2}{R_1 R_2 C_1}$$

$$\frac{2 \zeta}{\sqrt{R_1 R_2 C_1 C_2}} = \frac{R_1 + R_2}{R_1 R_2 C_1}$$

$$\zeta = \left(\frac{1}{2}\right) \left(\frac{R_1 + R_2}{R_1 R_2 C_1}\right) \sqrt{R_1 R_2 C_1 C_2}$$

$$\zeta = \frac{(R_1 + R_2)}{2} \sqrt{\frac{C_2}{R_1 R_2 C_1}}$$

Analytic
Equations

Analysis: Given R_1, R_2, C_1, C_2 Find w_n, ζ

Design: Given w_n, ζ Find R_1, R_2, C_1, C_2

There are infinite design solutions possible but only a limited set is practical. Generally:

- * R_1 OR R_2 should be greater than about 1k
- * R_1 OR R_2 should be less than about 1Meg
- * C_1 OR C_2 should be greater than about 300 pF
- * C_1 OR C_2 should be less than about 1uF

There are a number of possible design solutions.

A good example of a practical approach is contained within the spreadsheet `sk-des.xls`. The student will have to derive the math which is rather complicated — typical of design math.

SALLÉN-KEY LPF DESIGN


1/2

K. KUHN

FROM ANALYSIS:

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$
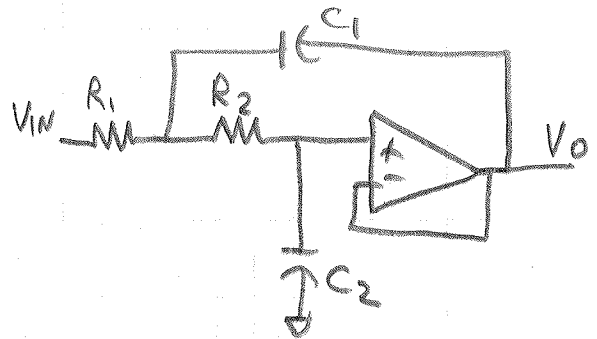
$$\zeta = \frac{R_1 + R_2}{2} \sqrt{\frac{C_2}{R_1 R_2 C_1}}$$



WE CAN WRITE:

$$\zeta^2 = \frac{(R_1 + R_2)^2}{4 R_1 R_2} \left(\frac{C_2}{C_1} \right) = \frac{R_1^2 + 2 R_1 R_2 + R_2^2}{4 R_1 R_2} \left(\frac{C_2}{C_1} \right)$$

$$= \left(\frac{R_1}{4 R_2} + \frac{1}{2} + \frac{R_2}{4 R_1} \right) \left(\frac{C_2}{C_1} \right)$$

$$= \left(\frac{1}{4 (R_2/R_1)} + \frac{1}{2} + \frac{(R_2/R_1)}{4} \right) \left(\frac{C_2}{C_1} \right)$$

$$\left(\frac{R_2}{R_1} \right) \zeta^2 = \left(\frac{1}{4} + \frac{R_2/R_1}{2} + \frac{(R_2/R_1)^2}{4} \right) \left(\frac{C_2}{C_1} \right)$$

$$\left(\frac{C_2/C_1}{4} \right) \left(\frac{R_2}{R_1} \right)^2 + \left(\frac{C_2/C_1}{2} - \zeta^2 \right) \left(\frac{R_2}{R_1} \right) + \frac{C_2/C_1}{4} = 0$$

$$\frac{R_2}{R_1} = \frac{\zeta^2 - \frac{C_2/C_1}{2} \pm \sqrt{\left(\frac{C_2/C_1}{2} - \zeta^2 \right)^2 - \frac{(C_2/C_1)^2}{4}}}{\left(\frac{C_2/C_1}{4} \right)}$$

$$\frac{R_2}{R_1} = \frac{2\delta^2 - \frac{C_2}{C_1} + 2\sqrt{\frac{(C_2/C_1)^2}{4} - \frac{2(C_2/C_1)\delta^2 + \delta^4}{2}} - \frac{(C_2/C_1)^2}{4}}{(C_2/C_1)}$$

$$\frac{R_2}{R_1} = \frac{2\delta^2 - \left(\frac{C_2}{C_1}\right) + 2\delta\sqrt{\delta^2 - \left(\frac{C_2}{C_1}\right)}}{(C_2/C_1)}$$

NOTE:

$$\frac{C_2}{C_1} \leq \delta^2 \text{ for real sqrt}$$

PROCEDURE:

① DETERMINE $C = \sqrt{C_1 C_2} = \frac{4 \times 10^{-7}}{\sqrt{\text{Frequency (Hz)}}}$ Farads

② $C_1 = C/\delta$ and round C_1 to near std value

③ $C_2 < \delta^2 C_1$ and round C_2 down to convenient std value

④ $K = \frac{R_2}{R_1} = \frac{2\delta^2 - \left(\frac{C_2}{C_1}\right) + 2\delta\sqrt{\delta^2 - \frac{C_2}{C_1}}}{C_2/C_1}$


⑤ $R^2 = R_1 R_2 = \frac{1}{\omega_n^2 C_1 C_2}$

⑥ $K R_1^2 = R^2 \therefore R_1 = \sqrt{\frac{R^2}{K}}$ round to closest std value

⑦ $R_2 = \frac{R^2}{R_1}$ round to closest std value

INVERTING SECOND ORDER LOW-PASS FILTER

K. KUHN
1-23-00

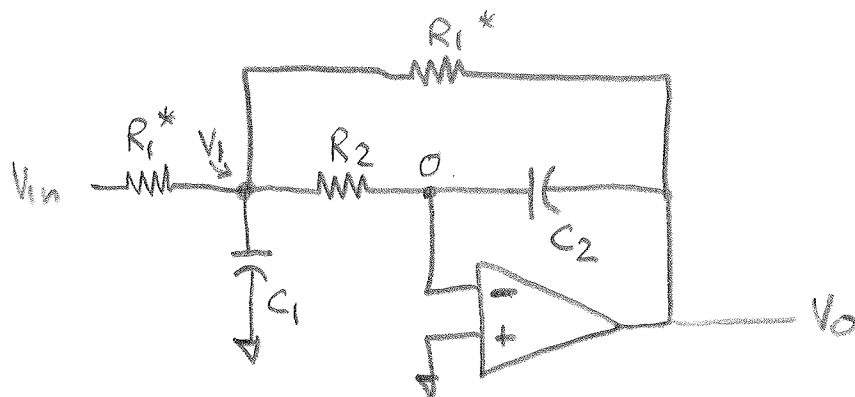

* THE TWO RESISTORS ARE EQUAL FOR (INVERTED) UNITY GAIN AT DC

$$V_1 = \frac{V_{in} (R_1 \parallel R_2) \parallel \frac{1}{C_1 s}}{R_1 + (R_1 \parallel R_2) \parallel \frac{1}{C_1 s}} + \frac{V_o (R_1 \parallel R_2) \parallel \frac{1}{C_1 s}}{R_1 + (R_1 \parallel R_2) \parallel \frac{1}{C_1 s}}$$

$$\begin{aligned} -(R_1 \parallel R_2) \parallel \frac{1}{C_1 s} &= \frac{\frac{R_1 \parallel R_2}{C_1 s}}{R_1 \parallel R_2 + \frac{1}{C_1 s}} = \frac{R_1 \parallel R_2}{(R_1 \parallel R_2) C_1 s + 1} \\ &= \frac{R_1 R_2}{R_1 R_2 C_1 s + R_1 + R_2} \end{aligned}$$

$$V_1 = \frac{(V_{in} + V_o) R_1 R_2}{R_1 (R_1 R_2 C_1 s + R_1 + R_2) + R_1 R_2} = \frac{(V_{in} + V_o) R_2}{R_1 R_2 C_1 s + R_1 + 2 R_2}$$

$$V_o = \frac{-V_1}{R_2 C_2 s} \quad \therefore V_1 = -V_o R_2 C_2 s$$

$$-V_o R_2 C_2 s = \frac{(V_{in} + V_o) R_2}{R_1 R_2 C_1 s + R_1 + 2 R_2}$$

$$(-V_o R_2 C_2 s)(R_1 R_2 C_1 s + R_1 + 2R_2) = (V_{in} + V_o) R_2$$

$$-V_o [R_1 R_2 C_1 C_2 s^2 + (R_1 + 2R_2) C_2 s] = V_{in} + V_o$$

$$\frac{V_o}{V_{in}} = \frac{-1}{R_1 R_2 C_1 C_2 s^2 + (R_1 + 2R_2) C_2 s + 1}$$

$$= \frac{-1/R_1 R_2 C_1 C_2}{s^2 + \frac{(R_1 + 2R_2) C_2 s}{R_1 R_2 C_1 C_2} + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$\frac{V_o}{V_{in}} = \frac{-1/R_1 R_2 C_1 C_2}{s^2 + \frac{(R_1 + 2R_2) C_2 s}{R_1 R_2 C_1 C_2} + \frac{1}{R_1 R_2 C_1 C_2}} \Rightarrow \frac{-\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \quad (\text{std. form})$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$2\zeta\omega_n = \frac{R_1 + 2R_2}{R_1 R_2 C_1}$$


$$\zeta = \frac{\frac{R_1 + 2R_2}{R_1 R_2 C_1}}{2} * \sqrt{R_1 R_2 C_1 C_2} = \left(\frac{R_1}{2} + R_2\right) \sqrt{\frac{R_1 R_2 C_1 C_2}{R_1^2 R_2^2 C_1^2}}$$

$$= \left(\frac{R_1}{2} + R_2\right) \sqrt{\frac{C_2}{R_1 R_2 C_1}}$$

$$\zeta = \left(\frac{\frac{R_1}{2} + R_2}{\sqrt{R_1 R_2}}\right) \sqrt{\frac{C_2}{C_1}}$$

NON-INVERTED SECOND ORDER HIGH-PASS FILTER

K. KUHN
1-23-00

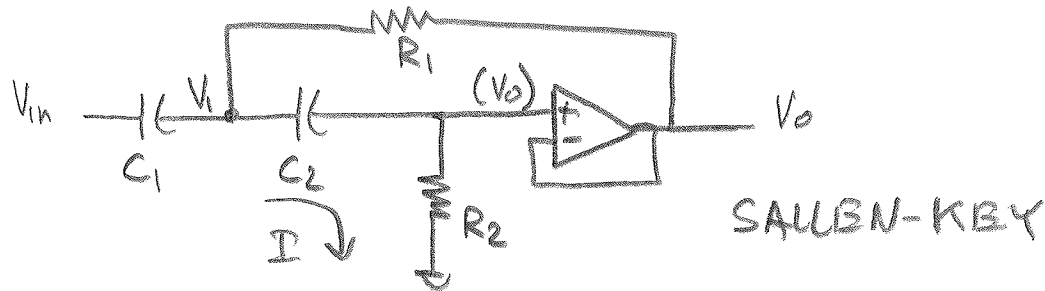

$$\frac{V_{in} - V_1}{1/C_1 s} = \frac{V_1 - V_o}{R_1} + \frac{V_1 - V_o}{1/C_2 s}$$

$$I = \frac{V_o}{R_2}$$

$$V_1 = V_o + \frac{I}{C_2 s} = V_o \left[1 + \frac{1}{R_2 C_2 s} \right] = V_o \left[\frac{R_2 C_2 s + 1}{R_2 C_2 s} \right]$$

$$\frac{V_{in} - V_o \left[\frac{R_2 C_2 s + 1}{R_2 C_2 s} \right]}{1/C_1 s} = \frac{V_o \left[\frac{R_2 C_2 s + 1}{R_2 C_2 s} \right] - V_o}{R_1} + \frac{V_o}{R_2}$$

$$V_o \left[\left[\frac{R_2 C_2 s + 1}{R_2 C_2 s} \right] C_1 s + \frac{R_2 C_2 s + 1}{R_1 R_2 C_2 s} - \frac{1}{R_1} + \frac{1}{R_2} \right] = V_{in} C_1 s$$

$$V_o \left[\frac{R_1 C_1 s (R_2 C_2 s + 1) + R_2 C_2 s + 1 - R_2 C_2 s + R_1 C_2 s}{R_1 R_2 C_2 s} \right] = V_{in} C_1 s$$

$$V_o \left[\frac{R_1 R_2 C_1 C_2 s^2 + R_1 C_1 s + \cancel{R_2 C_2 s + 1} - \cancel{R_2 C_2 s} + R_1 C_2 s}{R_1 R_2 C_2 s} \right] = V_{in} C_1 s$$

$$\frac{V_o}{V_{in}} = \frac{R_1 R_2 C_1 C_2 s^2}{R_1 R_2 C_1 C_2 s^2 + R_1 (C_1 + C_2) s + 1}$$

$$\frac{V_o}{V_{in}} = \frac{s^2}{s^2 + \frac{R_1 (C_1 + C_2) s}{R_1 R_2 C_1 C_2} + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$\frac{V_o}{V_{in}} = \frac{s^2}{s^2 + \frac{(C_1 + C_2) s}{R_2 C_1 C_2} + \frac{1}{R_1 R_2 C_1 C_2}} \Rightarrow \frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

std form


$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$2\zeta\omega_n = \frac{(C_1 + C_2)}{R_2 C_1 C_2}$$

$$\zeta = \frac{(C_1 + C_2) \sqrt{R_1 R_2 C_1 C_2}}{2 R_2 C_1 C_2} = \zeta = \frac{1}{2} \sqrt{\frac{R_1}{R_2}} \sqrt{\frac{(C_1 + C_2)^2}{C_1 C_2}}$$

INVERTING SECOND ORDER HIGH-PASS FILTER

K. KUHN
1-23-00

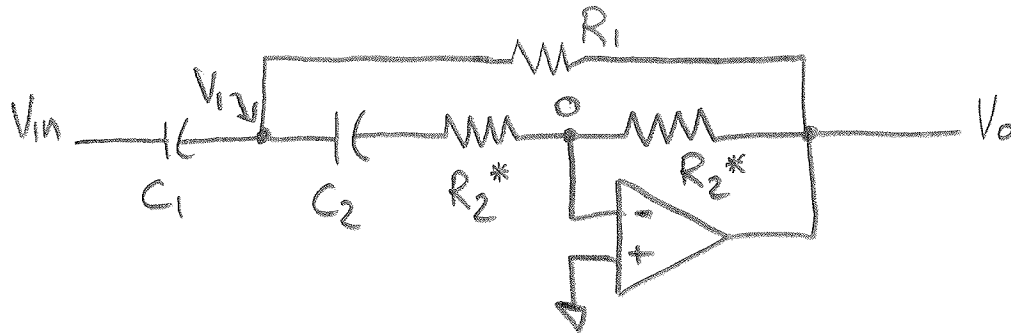

*THE TWO RESISTORS ARE EQUAL FOR (INVERTED) UNITY GAIN AT HIGH FREQUENCIES

$$\text{IMPEDANCE } \frac{1}{C_2 s} + R_2 = \frac{R_2 C_2 s + 1}{C_2 s}$$

$$V_1 = V_{in} \left[\frac{R_1 \parallel \left(\frac{R_2 C_2 s + 1}{C_2 s} \right)}{\frac{1}{C_1 s} + R_1 \parallel \left(\frac{R_2 C_2 s + 1}{C_2 s} \right)} \right] + \frac{V_o \left[\frac{1}{C_1 s} \parallel \left(\frac{R_2 C_2 s + 1}{C_2 s} \right) \right]}{R_1 + \frac{1}{C_1 s} \parallel \left(\frac{R_2 C_2 s + 1}{C_2 s} \right)}$$

$$R_1 \parallel \left(\frac{R_2 C_2 s + 1}{C_2 s} \right) = \frac{R_1 \left(\frac{R_2 C_2 s + 1}{C_2 s} \right)}{R_1 + \frac{R_2 C_2 s + 1}{C_2 s}} = \frac{R_1 (R_2 C_2 s + 1)}{R_1 C_2 s + R_2 C_2 s + 1}$$

$$= \frac{R_1 (R_2 C_2 s + 1)}{(R_1 + R_2) C_2 s + 1}$$

$$\frac{1}{C_1 s} \parallel \left(\frac{R_2 C_2 s + 1}{C_2 s} \right) = \frac{\frac{R_2 C_2 s + 1}{C_1 C_2 s^2}}{\frac{1}{C_1 s} + \frac{R_2 C_2 s + 1}{C_2 s}} = \frac{R_2 C_2 s + 1}{C_2 s + R_2 C_1 C_2 s^2 + C_1 s}$$

$$= \frac{R_2 C_2 s + 1}{R_2 C_1 C_2 s^2 + (C_1 + C_2) s}$$



$$\begin{aligned}
 V_1 &= \frac{\frac{V_{in} R_1 (R_2 C_2 s + 1)}{(R_1 + R_2) C_2 s + 1}}{\frac{1}{C_1 s} + \frac{R_1 (R_2 C_2 s + 1)}{(R_1 + R_2) C_2 s + 1}} + \frac{\frac{V_o (R_2 C_2 s + 1)}{R_2 C_1 C_2 s^2 + (C_1 + C_2) s}}{R_1 + \frac{R_2 C_2 s + 1}{R_2 C_1 C_2 s^2 + (C_1 + C_2) s}} \\
 &= \frac{\frac{V_{in} R_1 (R_2 C_2 s + 1)}{(R_1 + R_2) C_2 s + 1} + \frac{V_o (R_2 C_2 s + 1)}{R_1 (R_2 C_1 C_2 s^2 + (C_1 + C_2) s) + R_2 C_2 s + 1}}{C_1 s} \\
 &= \frac{V_{in} R_1 C_1 s (R_2 C_2 s + 1)}{(R_1 + R_2) C_2 s + 1 + R_1 C_1 s (R_2 C_2 s + 1)} + \frac{V_o (R_2 C_2 s + 1)}{R_1 (R_2 C_1 C_2 s^2 + (C_1 + C_2) s) + R_2 C_2 s + 1} \\
 &= \frac{V_{in} R_1 C_1 s (R_2 C_2 s + 1) + V_o (R_2 C_2 s + 1)}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_1 C_2 + R_2 C_2) s + 1} \quad \left(\begin{array}{l} \text{DENOMINATORS} \\ \text{ARE THE SAME} \\ \text{WHEN EXPANDED} \end{array} \right)
 \end{aligned}$$

$$V_o = \frac{-V_1 R_2}{\frac{R_2 C_2 s + 1}{C_2 s}} = \frac{-V_1 R_2 C_2 s}{R_2 C_2 s + 1} \quad \therefore V_1 = \frac{-V_o (R_2 C_2 s + 1)}{R_2 C_2 s}$$

$$\frac{-V_o \cancel{(R_2 C_2 s + 1)}}{R_2 C_2 s} = \frac{V_{in} R_1 C_1 s \cancel{(R_2 C_2 s + 1)} + V_o \cancel{(R_2 C_2 s + 1)}}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_1 C_2 + R_2 C_2) s + 1}$$

$$-V_o \left[\frac{1}{R_2 C_2 s} + \frac{R_2 C_2 s}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_1 C_2 + R_2 C_2) s + 1} \right] = \frac{V_{in} R_1 C_1 s}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_1 C_2 + R_2 C_2) s + 1}$$

$$-V_o \left[1 + \frac{R_2 C_2 s}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_1 C_2 + R_2 C_2) s + 1} \right] = \frac{V_{in} R_1 R_2 C_1 C_2 s^2}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_1 C_2 + R_2 C_2) s + 1}$$

$$-V_o \left[\frac{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_1 C_2 + 2R_2 C_2)s + 1}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_1 C_2 + 2R_2 C_2)s + 1} \right] = \frac{V_i R_1 R_2 C_1 C_2 s^2}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_1 C_2 + 2R_2 C_2)s + 1}$$

$$\frac{V_o}{V_{in}} = \frac{-R_1 R_2 C_1 C_2 s^2}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_1 C_2 + 2R_2 C_2)s + 1}$$

$$\frac{V_o}{V_{in}} = \frac{-s^2}{s^2 + \frac{(R_1 C_1 + R_1 C_2 + 2R_2 C_2)s}{R_1 R_2 C_1 C_2} + \frac{1}{R_1 R_2 C_1 C_2}} \Rightarrow \frac{-s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

std. form

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$


$$2\zeta\omega_n = \frac{(R_1 C_1 + R_1 C_2 + 2R_2 C_2)}{R_1 R_2 C_1 C_2}$$

$$\zeta = \frac{(R_1 C_1 + R_1 C_2 + 2R_2 C_2) \sqrt{R_1 R_2 C_1 C_2}}{2 R_1 R_2 C_1 C_2}$$

$$\zeta = \frac{R_1 C_1 + R_1 C_2 + 2R_2 C_2}{2 \sqrt{R_1 R_2 C_1 C_2}}$$

NON-INVERTING SECOND-ORDER BAND-PASS FILTER

K. KUHN
1-23-00

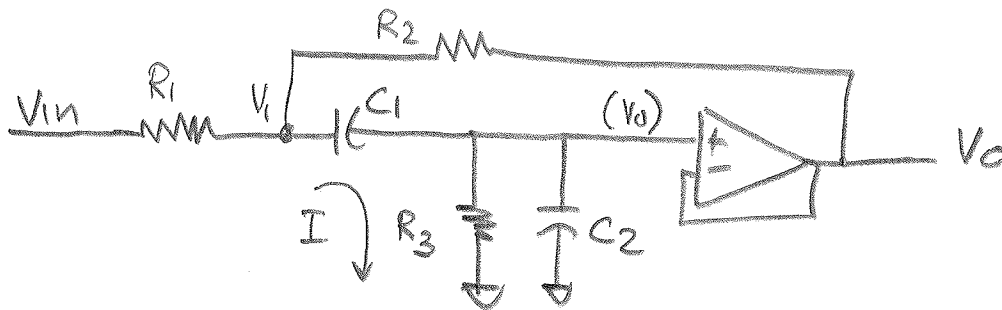

$$\frac{V_{in} - V_0}{R_1} = \frac{V_1 - V_0}{R_2} + \frac{V_1 - V_0}{1/C_1 s}$$

$$R_3 \parallel \frac{1}{C_2 s} = \frac{R_3 / C_2 s}{R_3 + 1/C_2 s} = \frac{R_3}{R_3 C_2 s + 1}$$

$$I = \frac{V_0 (R_3 C_2 s + 1)}{R_3}$$

$$V_1 = V_0 + \frac{I}{C_1 s} = V_0 \left[1 + \frac{R_3 C_2 s + 1}{R_3 C_1 s} \right] = V_0 \left[\frac{R_3 (C_1 + C_2) s + 1}{R_3 C_1 s} \right]$$

$$\frac{V_{in} - V_0 \left[\frac{R_3 (C_1 + C_2) s + 1}{R_3 C_1 s} \right]}{R_1} = \frac{V_0 \left[\frac{R_3 (C_1 + C_2) s + 1}{R_3 C_1 s} \right] - V_0 + \frac{V_0 (R_3 C_2 s + 1)}{R_3}}{R_2}$$

$$V_0 \left[\frac{R_3 (C_1 + C_2) s + 1}{R_1 R_3 C_1 s} + \frac{R_3 (C_1 + C_2) s + 1}{R_2 R_3 C_1 s} - \frac{1}{R_2} + \frac{R_3 C_2 s + 1}{R_3} \right] = \frac{V_{in}}{R_1}$$

$$V_0 \left[\frac{R_2 R_3 (C_1 + C_2) s + R_2 + R_1 R_3 (C_1 + C_2) s + R_1 - R_1 R_3 C_1 s + R_1 R_2 R_3 C_1 C_2 s^2 + R_1 R_2 C_1 s}{R_1 R_2 R_3 C_1 s} \right] = \frac{V_{in}}{R_1}$$

$$V_o \left[\frac{R_1 R_2 R_3 C_1 C_2 s^2 + (R_2 R_3 C_1 + R_2 R_3 C_2 + R_1 R_3 C_1 + R_1 R_3 C_2 - R_1 R_3 C_1 + R_1 R_2 C_1) s + R_1 + R_2}{R_2 R_3 C_1 s} \right] = V_{in}$$

$$\frac{V_o}{V_{in}} = \frac{R_2 R_3 C_1 s}{R_1 R_2 R_3 C_1 C_2 s^2 + (R_1 R_2 C_1 + R_1 R_3 C_2 + R_2 R_3 C_1 + R_2 R_3 C_2) s + R_1 + R_2}$$

$$= \frac{\cancel{R_2 R_3 C_1} s / \cancel{R_1 R_2 R_3 C_1 C_2}}{s^2 + \frac{(R_1 R_2 C_1 + R_1 R_3 C_2 + R_2 R_3 C_1 + R_2 R_3 C_2) s}{R_1 R_2 R_3 C_1 C_2} + \frac{R_1 + R_2}{R_1 R_2 R_3 C_1 C_2}}$$

$$\frac{V_o}{V_{in}} = \frac{s / R_1 C_2}{s^2 + \frac{(R_1 R_2 C_1 + R_1 R_3 C_2 + R_2 R_3 C_1 + R_2 R_3 C_2) s}{R_1 R_2 R_3 C_1 C_2} + \frac{R_1 + R_2}{R_1 R_2 R_3 C_1 C_2}}$$

THE PEAK RESPONSE AT $\omega = \omega_n$


$$= \frac{1}{\cancel{R_1 C_2}} \times \frac{\cancel{R_1 R_2 R_3 C_1 C_2}}{R_1 R_2 C_1 + R_1 R_3 C_2 + R_2 R_3 C_1 + R_2 R_3 C_2}$$

$$= \frac{1}{\frac{R_1}{R_2} + \frac{R_1 C_2}{R_2 C_1} + 1 + \frac{C_2}{C_1}}$$

$$= \frac{1}{\frac{R_1}{R_3} + \left(1 + \frac{R_1}{R_2}\right) \frac{C_2}{C_1}}$$

INVERTING SECOND ORDER BAND-PASS FILTER

K. KUHN
1-23-00

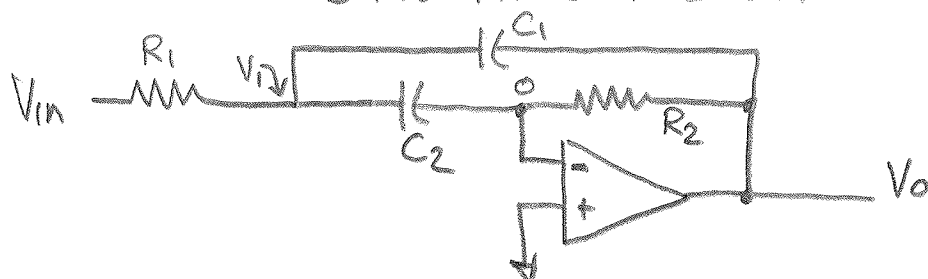

$$\frac{1}{C_1 s} \parallel \frac{1}{C_2 s} = \frac{\frac{1}{C_1 s} \frac{1}{C_2 s}}{\frac{1}{C_1 s} + \frac{1}{C_2 s}} = \frac{1}{(C_1 + C_2)s}$$

$$R_1 \parallel \frac{1}{C_2 s} = \frac{\frac{R_1}{C_2 s}}{R_1 + \frac{1}{C_2 s}} = \frac{R_1}{R_1 C_2 s + 1}$$

$$V_i = \frac{V_{in} \left(\frac{1}{(C_1 + C_2)s} \right)}{R_1 + \frac{1}{(C_1 + C_2)s}} + \frac{V_o \left(\frac{R_1}{R_1 C_2 s + 1} \right)}{\frac{1}{C_1 s} + \frac{R_1}{R_1 C_2 s + 1}}$$

$$= \frac{V_{in}}{R_1 (C_1 + C_2)s + 1} + \frac{V_o R_1}{\frac{R_1 C_2 s + 1}{C_1 s} + R_1}$$

$$= \frac{V_{in}}{R_1 (C_1 + C_2)s + 1} + \frac{V_o R_1 C_1 s}{R_1 (C_1 + C_2)s + 1}$$

$$V_o = -V_i R_2 C_2 s \quad \therefore \quad V_i = \frac{-V_o}{R_2 C_2 s}$$

$$\frac{-V_o}{R_2 C_2 s} = \frac{V_{in}}{R_1 (C_1 + C_2)s + 1} + \frac{V_o R_1 C_1 s}{R_1 (C_1 + C_2)s + 1}$$

$$-V_o \left[\frac{1}{R_2 C_2 s} + \frac{R_1 C_1 s}{R_1 (C_1 + C_2) s + 1} \right] = \frac{V_{in}}{R_1 (C_1 + C_2) s + 1}$$

$$-V_o \left[1 + \frac{R_1 R_2 C_1 C_2 s^2}{R_1 (C_1 + C_2) s + 1} \right] = \frac{V_{in} R_2 C_2 s}{R_1 (C_1 + C_2) s + 1}$$

$$-V_o \left[\frac{R_1 R_2 C_1 C_2 s^2 + R_1 (C_1 + C_2) s + 1}{R_1 (C_1 + C_2) s + 1} \right] = \frac{V_{in} R_2 C_2 s}{R_1 (C_1 + C_2) s + 1}$$

$$\frac{V_o}{V_{in}} = \frac{-R_2 C_2 s}{R_1 R_2 C_1 C_2 s^2 + R_1 (C_1 + C_2) s + 1} = \frac{-R_2 C_2 s / R_1 R_2 C_1 C_2}{\frac{s^2 + \frac{R_1 (C_1 + C_2) s}{R_1 R_2 C_1 C_2} + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$\frac{V_o}{V_{in}} = \frac{-s / R_1 C_1}{\frac{s^2 + \frac{(C_1 + C_2) s}{R_2 C_1 C_2} + \frac{1}{R_1 R_2 C_1 C_2}}{R_2 C_1 C_2}} \Rightarrow \frac{-2\zeta \omega_n s}{s^2 + 2\zeta \omega_n s + \omega_n^2}$$

std. form

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$2\zeta \omega_n = \frac{C_1 + C_2}{R_2 C_1 C_2}$$

$$\zeta = \frac{(C_1 + C_2) \sqrt{R_1 R_2 C_1 C_2}}{2 R_2 C_1 C_2} = \zeta = \frac{1}{2} \sqrt{\frac{R_1}{R_2}} \sqrt{\frac{(C_1 + C_2)^2}{C_1 C_2}}$$

$$2\zeta \omega_n K = \frac{1}{R_1 C_1}$$

$$K = \frac{\frac{1}{R_1 C_1}}{\frac{(C_1 + C_2)}{R_2 C_1 C_2}} = \frac{1}{R_1 C_1} \cdot \frac{R_2 C_1 C_2}{C_1 + C_2} = \frac{R_2 C_2}{R_1 (C_1 + C_2)} = K = \left(\frac{R_2}{R_1} \right) \left(\frac{1}{1 + \frac{C_1}{C_2}} \right)$$

THE PEAK MAGNITUDE RESPONSE AT $\omega = \omega_n$ IS K
 AN ALTERNATE REPRESENTATION OF K IS:

$$K = \frac{1}{R_1 C_1} + \frac{R_2 C_1 C_2}{C_1 + C_2} = \frac{1}{C_1} \left(\frac{R_2}{R_1} \right) \left(\frac{C_1 C_2}{C_1 + C_2} \right)$$

NOTE THAT


$$\zeta^2 = \frac{1}{4} \left(\frac{R_1}{R_2} \right) \left(\frac{(C_1 + C_2)^2}{C_1 C_2} \right)$$

THUS

$$K = \left(\frac{C_1 + C_2}{C_1} \right) \frac{1}{4\zeta^2} = \left(1 + \frac{C_2}{C_1} \right) \frac{1}{4\zeta^2} = \left(1 + \frac{C_2}{C_1} \right) Q^2$$

$(\zeta = \frac{1}{2Q})$

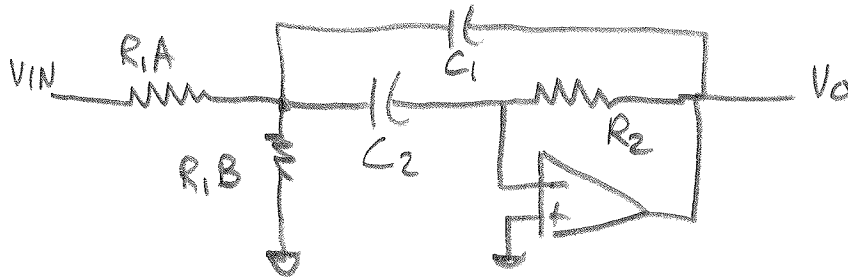IT IS SOMETIMES DESIRABLE TO ATTENUATE THE TRANSFER FUNCTION SO THAT THE PEAK RESPONSE IS 1.0. THE CIRCUIT IS MODIFIED AS FOLLOWS:



$$R_1 = R_{1A} \parallel R_{1B}$$

$$\frac{1}{K} = \frac{R_{1B}}{R_{1A} + R_{1B}} = \frac{1}{1 + \frac{R_{1A}}{R_{1B}}}$$

$$\frac{R_{1A}}{R_{1B}} = K - 1 \quad \therefore R_{1B} = \frac{R_{1A}}{K - 1}$$


$$R_1 = \frac{R_{1A} R_{1B}}{R_{1A} + R_{1B}} = \frac{R_{1A}}{K + 1}$$

$$R_{1A} = R_1 (K + 1)$$

$$R_{1B} = \frac{R_{1A}}{K - 1}$$

DESIGN NOTE FOR INVERTING BAND-PASS FILTER

JAN 23, 01
K. KUN

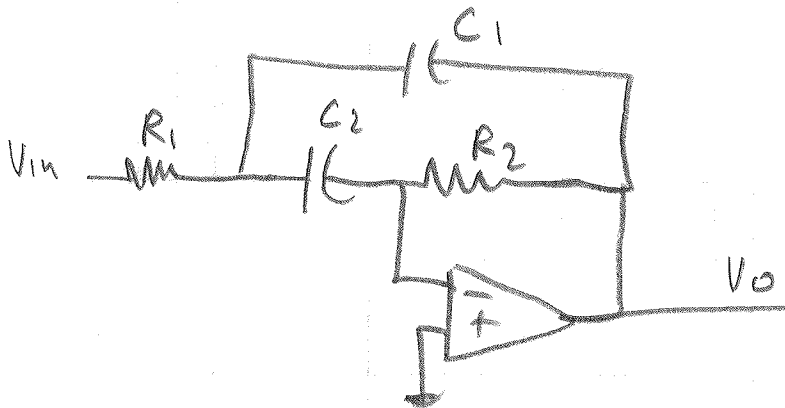

$$F = \frac{1}{2\pi\sqrt{R_1 R_2} C}$$

$$Q = \frac{1}{2} \sqrt{\frac{R_2}{R_1}}$$

1. LET $C_1 = C_2 = C \Rightarrow$ SELECTED APPROPRIATE STANDARD VALUE

2. $R = \frac{1}{2\pi F C}$

3. $R_1 = R/2Q \Rightarrow$ ROUNDED TO NEAREST STD VALUE


4. $R_2 = R * 2Q \Rightarrow$ " " " " " "

TRANSFER GAIN OF CIRCUIT AT RESONANT
FREQUENCY IS $-2Q^2$



BIQUAD FILTER

K. KUHN
2-4-01

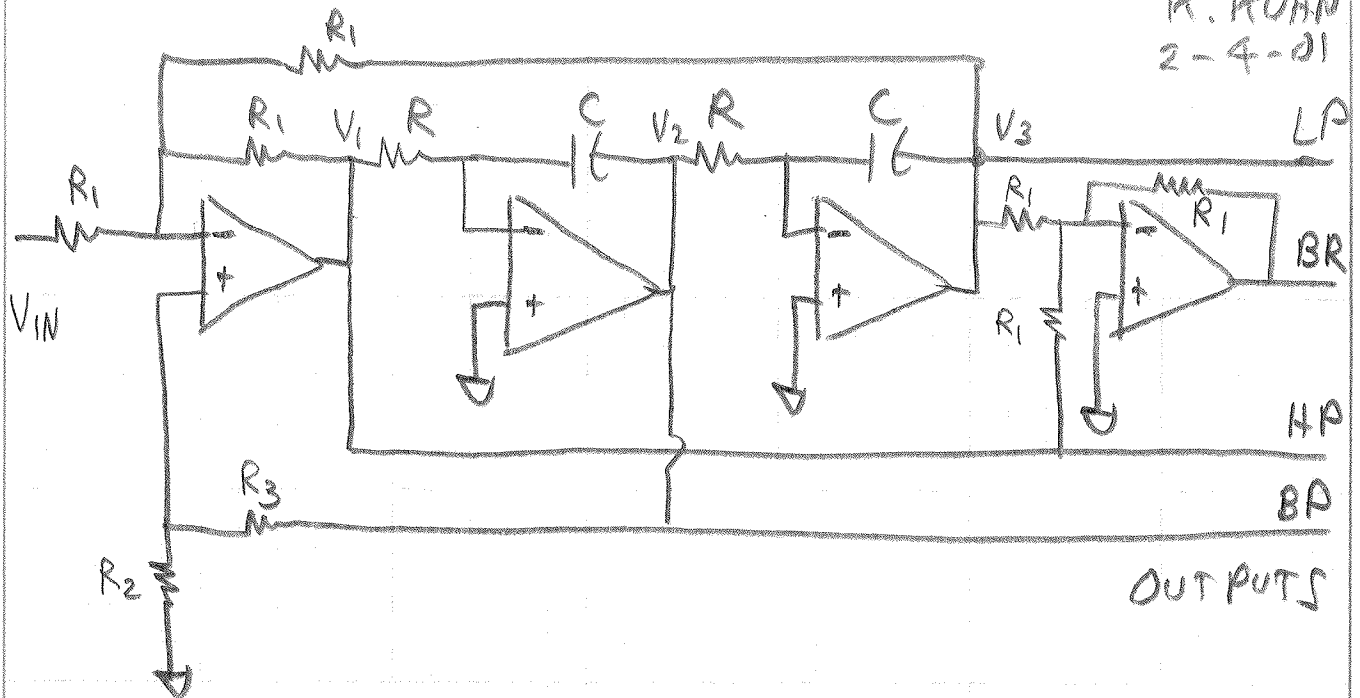

$$V_1 = -V_{IN} - V_3 + V_2 \left(\frac{R_2}{R_2 + R_3} \right) 3 = V_{HP}$$

$$V_2 = \frac{-V_1}{RCs} = V_{BP}$$

$$V_3 = \frac{-V_2}{RCs} = \frac{V_1}{R^2 C^2 s^2} = V_{LP}$$

$$V_{BR} = -V_1 - V_3$$

SOLVE FOR V_{HP} FIRST

$$V_{HP} = -V_{IN} - \frac{V_{HP}}{R^2 C^2 s^2} - \frac{V_{HP}}{RCs} \left(\frac{R_2}{R_2 + R_3} \right) 3$$

$$V_{HP} R^2 C^2 s^2 = -V_{IN} - V_{HP} - V_{HP} \left(\frac{R_2}{R_2 + R_3} \right) 3 RCs$$

$$V_{HP} \left(R^2 C^2 s^2 + 3 \left(\frac{R_2}{R_2 + R_3} \right) RCs + 1 \right) = -V_{IN} R^2 C^2 s^2$$

$$V_{HP} = \frac{-V_{IN} R^2 C^2 s^2}{R^2 C^2 s^2 + 3 \left(\frac{R_2}{R_2 + R_3} \right) RCs + 1}$$

$$V_{HP} = \frac{-V_{IN} s^2}{s^2 + \frac{3}{RC} \left(\frac{R_2}{R_2 + R_3} \right) s + \frac{1}{R^2 C^2}}$$

$$\omega_n = \frac{1}{RC}$$

$$2\zeta\omega_n = \frac{3}{RC} \left(\frac{R_2}{R_2 + R_3} \right)$$

$$\zeta = \frac{\frac{3}{RC} \left(\frac{R_2}{R_2 + R_3} \right)}{2\omega_n} = \frac{\frac{3}{RC} \left(\frac{R_2}{R_2 + R_3} \right)}{2/RC} = \frac{3}{2} \left(\frac{R_2}{R_2 + R_3} \right)$$

$$\zeta = \frac{3}{2} \left(\frac{1}{1 + R_3/R_2} \right)$$

$$\zeta \Rightarrow 0 \text{ AS } R_3/R_2 \Rightarrow \infty$$

$$\zeta \Rightarrow 1.5 \text{ AS } R_3/R_2 \Rightarrow 0$$

$$Q = \frac{1}{2\zeta} = \frac{1}{2 \left(\frac{3}{2} \right) \left(\frac{1}{1 + R_3/R_2} \right)}$$

$$Q = \frac{1 + \frac{R_3}{R_2}}{3}$$

$$3Q = 1 + R_3/R_2$$

$$\frac{R_3}{R_2} = 3Q - 1$$

The denominator in terms of Q

$$\begin{aligned}
 & s^2 + \frac{3}{RC} \left(\frac{1}{1 + \frac{R_2}{R_1}} \right) s + \frac{1}{R^2 C^2} \\
 &= s^2 + \frac{3}{RC} \left(\frac{1}{1 + 3Q - 1} \right) s + \frac{1}{R^2 C^2} \\
 &= s^2 + \frac{3}{RC} \left(\frac{1}{3Q} \right) s + \frac{1}{R^2 C^2} \\
 &= s^2 + \frac{s}{RCQ} + \frac{1}{R^2 C^2}
 \end{aligned}$$

$$V_{HP} = \frac{-V_{IN} s^2}{s^2 + \frac{s}{RCQ} + \frac{1}{R^2 C^2}}$$

$$V_{BP} = V_{HP} \left(\frac{-1}{RCs} \right)$$

$$V_{BP} = \frac{V_{IN} s / RC}{s^2 + \frac{s}{RCQ} + \frac{1}{R^2 C^2}}$$

$$V_{LP} = V_{BP} \left(\frac{-1}{RCs} \right)$$

$$V_{LP} = \frac{-V_{IN} / R^2 C^2}{s^2 + \frac{s}{RCQ} + \frac{1}{R^2 C^2}}$$

$$V_{BR} = -V_{HP} - V_{LP} = \frac{-(-V_{IN} s^2)}{s^2 + \frac{s}{RCQ} + \frac{1}{R^2 C^2}} - \frac{(-V_{IN} / R^2 C^2)}{s^2 + \frac{s}{RCQ} + \frac{1}{R^2 C^2}}$$

$$V_{BR} = \frac{V_{IN} (s^2 + 1/R^2 C^2)}{s^2 + \frac{s}{RCQ} + \frac{1}{R^2 C^2}}$$

MAGNITUDE OF TRANSFER FUNCTION

AT $s = 1/RC$:

$$\left| \frac{V_{HP}}{V_{IN}} \right|_{s=1/RC} = Q$$

$$\left| \frac{V_{BP}}{V_{IN}} \right|_{s=1/RC} = Q$$

$$\left| \frac{V_{LP}}{V_{IN}} \right|_{s=1/RC} = Q$$

$$\left| \frac{V_{BR}}{V_{IN}} \right|_{s=1/RC} = 0$$

Q	R_3/R_2
1	2
2	5
5	14
10	29
20	59
50	149
100	299