

EE351 Test1 2016						
Problem 1:						
0.1	Vs	0.625	input voltage divider			
600	Rs	0.769	voltage divider to stage 2			
1,000	Rin1	0.690	voltage divider to load			
250	Av1	112.7	voltage gain (loaded)			
1,500	Ro1	317,713	power gain			
5,000	Rin2	55.0	dB power gain			
0.85	Av2					
18	Ro2					
40	RL					
Problem 2:						
0.700	Vd	0.0259	kT/q	0.026		
300	T	10.5E-3	I			
15.0E-9	Is	4.9	rd			
2.0	n					
Problem 3:						
5	V1	Forward	D1			
8	V2	Reverse	D2			
Problem 4:						
		0.705	VBE _{max}		160	RE chosen
2200	Ro	0.529	VBE _{min}	3,996	RB	
-30	Av	1.585	VBB min	12.618	VCC/VBB	
20	VCC	0.617	VBE _{nom}	11.618	(RB1/RB2)	
9	VCQ	24.974	(RB/RE) _{max}	50,421	RB1 calculated	
1.2	KT, KB	141	B _{nom}		51,000	RB1 chosen
80	T _{max}	2,200	RC	4,390	RB2 calculated	
0	T _{min}	5.000E-3	ICQ		4,300	RB2 chosen
0.65	VBE at 25C	5.035E-3	IEQ	67.7	RE' needed	
-0.0022	d VBE/C	163.6	RE calculated	117.2	RE1 calculated	
250	B _{max}	5.2	re		120	RE1 chosen
80	B _{min}	0.993	B/(B+1)			
Problem 5:						
VBE _{nom}	0.617	1.555	VBB	9.1	VCQ	
B _{nom}	141	3,966	RB	5.2	re	
0.026	VT	4.994E-3	IE	68.6	RE'	
3,000	RL	0.993	B/(B+1)	-29.6	Av	
		4.959E-3	IC	-17.1	Av _i	
Problem 6:						
0.008	IE	3.250	re			
0.026	VT	600	RE RL			
150	B	91,091	r _{bt}			
20,000	RB	16,399	R _{in}			
1,000	RE	0.995	Av _i			
1,500	RL					

